

→ Electromagnetic Forces

$$\vec{F} = m\vec{a}$$

 $\vec{F}_E$ : electric force

 $\vec{F}_{EM}$ : electromagnetic force

 $\vec{F}_B$ : magnetic force
→ Charges

1) charge is conserved

$$e^- + e^+ = \delta + \delta$$

photons have zero charge




2) charge is quantized (1 coulomb :  $\pm 1.6 \times 10^{-19} \text{ C}$ )→ Coulomb's Law

\* like charges repel

\* force acts along line joining charges

\* unlike charges attract

\*

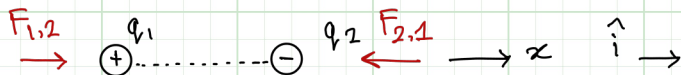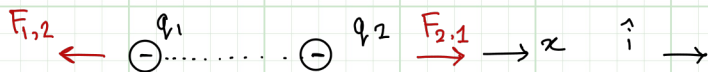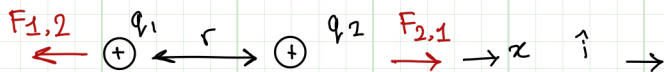Notes\*  $F_{2,1}$  is the force on charge 2 by charge 1.\*  $|\vec{F}_{2,1}| = |\vec{F}_{1,2}| = F_{1,2}$  ... no arrow

$$|\vec{F}_{1,2}| = |\vec{F}_{2,1}| = k \frac{|q_1||q_2|}{r^2}$$

$$k = 9 \times 10^9$$

$$k = \frac{1}{4\pi\epsilon_0}$$

$$\epsilon_0 = \text{permittivity of free space or vacuum} = 8.85 \times 10^{-12} \frac{C^2}{N \cdot m^2}$$

Units

$$q_1 = [C]$$

$$|\vec{F}_{1,2}| = k \frac{|q_1||q_2|}{r^2}$$

$$r = [m]$$

$$F = [N]$$

$$k = \left[ \frac{N \cdot m^2}{C^2} \right]$$

$$|\vec{F}_E| = \frac{1}{4\pi\epsilon_0} \frac{|q_1||q_2|}{r^2} \quad \epsilon_0 = 8.85 \times 10^{-12} \frac{C^2}{m^2 N} = \frac{\text{Farad}}{\text{metre}} = \frac{F}{m}$$

↑ permittivity of free space

$$F(x, y, z) = x^2 \hat{i} + 2xy \hat{j} + z \hat{k} \quad F: \mathbb{R}^3 \rightarrow \mathbb{R}^3$$

$$\left. \begin{aligned} f(x, y, z) &= x^2 + y^2 + z^2 \\ f(1, 1, 1) &= 3 \end{aligned} \right\} \text{scalar function}$$

### \* Magnitude and Direction

Physical Argument

Vectorial argument

$\hat{a}_r$  is a unit vector that points from source to the destination

### Example


Find location of  $q_0$  s.t.  $F_{\text{net}} = 0$

• we know  $q_0$  must be in the middle somewhere

• we know  $q_0$  should be closer to  $q$  because  $4q$  has more force

$$\left. \begin{aligned} |\vec{F}_{q_0, q}| &= \frac{1}{4\pi\epsilon_0} \cdot \frac{q q_0}{x^2} \\ |\vec{F}_{q_0, 4q}| &= \frac{1}{4\pi\epsilon_0} \cdot \frac{4q q_0}{(L-x)^2} \end{aligned} \right\} \frac{q q_0}{x^2} = \frac{4q q_0}{(L-x)^2} \Rightarrow x = L/3$$

### Example 2

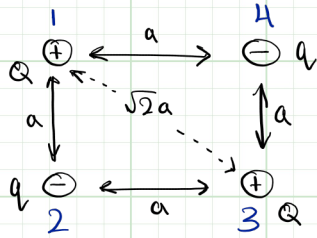

$$F_{1,3} = k \frac{Q^2}{2a^2}$$

$$\vec{F}_{1,3} = -\frac{kQ^2}{2a^2} \frac{1}{\sqrt{2}} \hat{i} + \frac{kQ^2}{2a^2} \frac{1}{\sqrt{2}} \hat{j}$$

$$\vec{F}_{1,2} = -\frac{kQ|q|}{a^2} \hat{j}$$

$$\vec{F}_{1,4} = \frac{kQ|q|}{a^2} \hat{i}$$

$$\vec{F}_{\text{net}} = \left[ -\frac{kQ^2}{2a^2} \cdot \frac{1}{\sqrt{2}} + \frac{kQ|q|}{a^2} \right] \hat{i} + \left[ \frac{kQ^2}{2a^2} \cdot \frac{1}{\sqrt{2}} - \frac{kQ|q|}{a^2} \right] \hat{j}$$


Set components equal to 0 and solve for  $\frac{Q}{|q|}$

$$\therefore \frac{Q}{|q|} = 2\sqrt{2}$$


Electric Field

Square system: Find  $\frac{Q}{|q|}$  s.t.  $\vec{F}_{1,\text{net}} = 0$
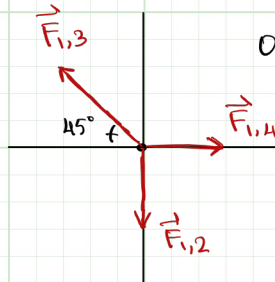
$$0 = \vec{F}_{1,2} + \vec{F}_{1,3} + \vec{F}_{1,4}$$





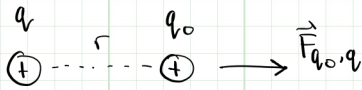

### Assumptions

- \*  $q_0$  is positive
- \*  $q_0$  is so small that it does not affect  $q$ 's field

$$\vec{E}_q = \frac{\vec{F}_{q_0, q}}{q_0}$$

\* field ~ change or modification of space


$$\vec{E}_q = \lim_{q_0 \rightarrow 0} \frac{\vec{F}_{q_0, q}}{q_0} \quad \left. \vphantom{\lim_{q_0 \rightarrow 0}} \right\} \text{limit def of } \vec{E}$$

$$|\vec{E}_q| = \frac{1}{4\pi\epsilon_0} \cdot \frac{|q||q_0|}{r^2} = \frac{1}{4\pi\epsilon_0} \cdot \frac{|q|}{r^2}$$

← magnitude of electric field at distance  $r$  from  $q$

$$|\vec{E}_q| = \frac{1}{4\pi\epsilon_0} \frac{|q|}{r^2}$$

### Direction

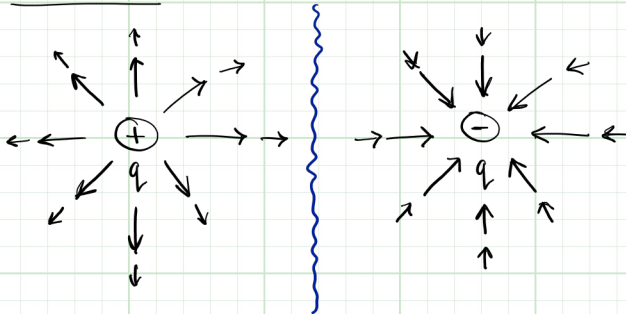


$$|\vec{E}_q| = \frac{1}{4\pi\epsilon_0} \frac{|q|}{r^2}$$

$$\vec{E}_q = \frac{\vec{F}_{q_0, q}}{q_0}$$

$$\vec{F}_{q_0, q} = q_0 \vec{E}_q$$

Electric field lines always start from positive charges and terminate at negative charges

### Force

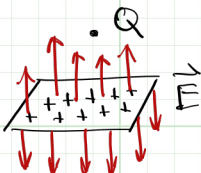

$$\vec{F}_Q = \vec{E} Q \quad \leftarrow \text{has an algebraic sign}$$


$\vec{E} \rightarrow \oplus Q \rightarrow \vec{F}_Q = \vec{E} Q$  (same direction as  $\vec{E}$ )  
 $\vec{E} \rightarrow \ominus Q \leftarrow \vec{F}_Q = \vec{E} (-Q)$  (opposite direction as  $\vec{E}$ )

- + A positive charge moves along  $\vec{E}$
- + A negative charge moves against  $\vec{E}$

### Units for Electric Field

$$\vec{E} = \left[ \frac{N}{C} \right] = \left[ \frac{\text{Volts}}{\text{metre}} \right] = \left[ \frac{V}{m} \right]$$

Example 1:

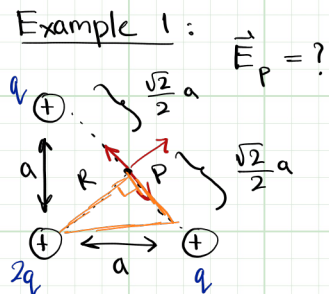


Superposition:

$$\vec{E}_T = \vec{E}_{2q} + \vec{E}_q + \vec{E}_{2q}$$

$$|\vec{E}_{2q}| = \frac{1}{4\pi\epsilon_0} \frac{2q}{R^2}$$

$$\vec{E}_{2q} = |\vec{E}_{2q}| \cos 45^\circ \hat{i} + |\vec{E}_{2q}| \sin 45^\circ \hat{j}$$

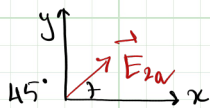

$$R^2 + \left( \frac{\sqrt{2}}{2} a \right)^2 = a^2$$

$$R^2 + \frac{2}{4} a^2 = a^2$$

$$R^2 = \frac{a^2}{2}$$

$$\therefore \vec{E}_{2q} = \frac{2q}{4\pi\epsilon_0} \frac{a^2}{2} \left[ \frac{1}{\sqrt{2}} \hat{i} + \frac{1}{\sqrt{2}} \hat{j} \right]$$

### Example 2

$$m_{\alpha} = 6.64 \times 10^{-27} \text{ kg}$$


charge of  $\alpha = 2e$

$$e = 1.602 \times 10^{-19} \text{ C}$$

$$\vec{F}_E = 2q\vec{E} = mg = \vec{F}_g$$

$$2q\vec{E} = mg$$

$$\vec{E} = \frac{mg}{2q}$$

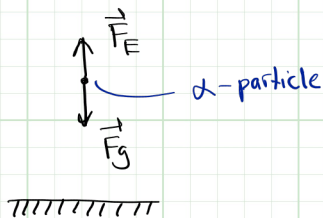

Gauss's Law (electric field)

is a subset of Maxwell Equations

electric flux

$$\oint_S \vec{E} \cdot d\vec{A} = \frac{Q_{enc}}{\epsilon_0}$$

enclosed charges (algebraic sign)

surface integral  
over a closed surface

differential surface element

encloses a volume




Differential Surface Element

$$\vec{A} = A \hat{n}$$

unit vector normal to plane

follows RHR

magnitude

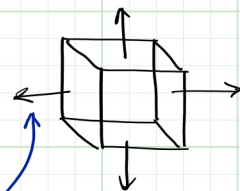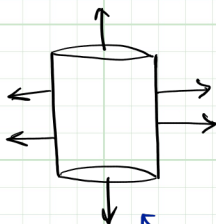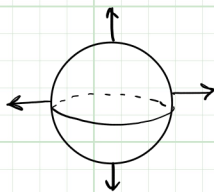

normal unit vectors  
always outward

$$d\vec{A}$$

$$= dA \hat{n}$$

normal  
unit vectors

tiny surface

## Double Integral

$$\int_{y_1}^{y_2} \int_{x_1}^{x_2} f(x)g(y) dx dy = \int_{y_1}^{y_2} g(y) dy \int_{x_1}^{x_2} f(x) dx = G(y) \Big|_{y_1}^{y_2} F(x) \Big|_{x_1}^{x_2}$$

Example  $\int_{y=0}^{y=1} \int_{x=1}^{x=2} 3xy^2 dx dy = 3 \int_{y=0}^{y=1} y^2 dy \int_{x=1}^{x=2} x dx$


$$= 3 \left( \frac{1}{3} y^3 \right) \Big|_0^1 \left( \frac{x^2}{2} \right) \Big|_1^2$$

$$= 3 \left( \frac{1}{3} \left( \frac{2^2}{2} - \frac{1^2}{2} \right) \right)$$

$$= 3 \left( \frac{1}{3} \times \frac{3}{2} \right) = 3 \left( \frac{3}{6} \right) = \boxed{\frac{3}{2}}$$



$$\text{Area} = ab$$

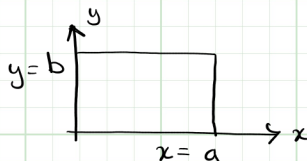


$$\int_{y=0}^{y=b} \int_{x=0}^{x=a} dx dy = \int_{y=0}^{y=b} dy \int_{x=0}^{x=a} dx = a \int_{y=0}^{y=b} dy = ab$$



$$\text{Area} = \pi r^2$$
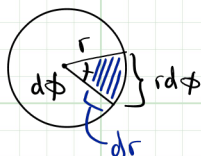
$$\int_{r=0}^{r=R} \int_{\phi=0}^{\phi=2\pi} r dr d\phi = \int_{r=0}^R r dr [\phi]_0^{2\pi}$$




$$= 2\pi \int_{r=0}^R r dr = 2\pi \left( \frac{r^2}{2} \right) \Big|_0^R = \pi R^2$$

## Surface Integral Trick

$$\begin{aligned}\iint_S \vec{E} \cdot d\vec{A} &= \iint |\vec{E}| |d\vec{A}| \cos \angle \vec{E}, d\vec{A} \\ &= \iint E dA \cos \angle \vec{E}, \hat{n} \quad \leftarrow \text{assuming } \vec{E} \text{ uniform and angle remains the same.} \\ &= E \cos \angle \vec{E}, \hat{n} \iint d\vec{A} = \frac{Q_{\text{enc}}}{\epsilon_0} \\ &= E \cdot \text{area} \cdot \cos \angle \vec{E}, \hat{n} = \frac{Q_{\text{enc}}}{\epsilon_0}\end{aligned}$$

### Example

$$\Phi_E = ?$$

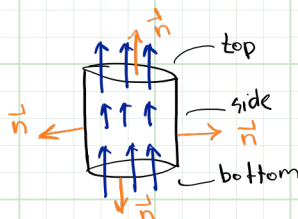

Electric flux  $\Phi_E = 0$   
because whatever going in goes out.

$$\begin{aligned}\iint \vec{E} \cdot d\vec{A} &= \iint_{\text{bottom}} \vec{E} \cdot d\vec{A} + \iint_{\text{top}} \vec{E} \cdot d\vec{A} + \iint_{\text{side}} \vec{E} \cdot d\vec{A} \\ &= \iint_{\text{bottom}} E dA \cos \angle \vec{E}, \hat{n} + \iint_{\text{top}} E dA \cos \angle \vec{E}, \hat{n} + \iint_{\text{side}} E dA \cos \angle \vec{E}, \hat{n} \\ &= E(-1) dA + E(1) dA + E(0) dA \\ &= E(-1) A_{\text{bot}} + E(1) A_{\text{top}} + E(0) = 0\end{aligned}$$

## Charge Density

- Linear charge distribution:  $Q = \int \lambda ds$  [C/m] ← diff. length
- Surface charge distribution:  $Q = \iint \sigma dA$  [C/m<sup>2</sup>] ← diff. area
- Volume charge distribution:  $Q = \iiint \rho dv$  [C/m<sup>3</sup>] ← diff. volume

## Application of Gauss Law

$$\textcircled{+} \frac{r}{r^2} E_q = \frac{kq}{r^2} = \frac{|q|}{4\pi\epsilon_0 r^2}$$


$$\iint_{GS} \vec{E} \cdot d\vec{A} = \frac{Q_{enc}}{\epsilon_0}$$

choose Gaussian surface wisely  
s.t.  $E$  and angle bt.  $E$  and  $\hat{n}$  are constant.

$$\iint_{GS} E \cos \angle \vec{E} \hat{n} dA = \frac{Q_{enc}}{\epsilon_0}$$

↳ can take out of integral

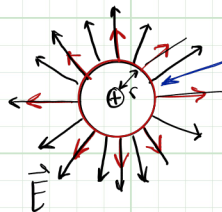- We can say point charge is symmetric sphere
- Therefore  $\vec{E}$  must be radially symmetric



Gaussian surface,  $\vec{E}$  is uniform and angle between  $\vec{E}$  and  $\hat{n}$  is same

$$\oiint \vec{E} \cdot d\vec{A} = \oiint E \underbrace{\cos \angle \vec{E} \hat{n}}_{\cos(0)=1} dA = E \oiint dA = \frac{Q}{\epsilon_0}$$




$$E \times \text{Surface Area} = \frac{Q}{\epsilon_0}$$

$$E \cdot 4\pi r^2 = \frac{Q}{\epsilon_0}$$

$$\vec{E}_q = \vec{E} Q \rightarrow \vec{E} = \frac{\vec{F}}{Q}$$

$$E = \frac{Q}{4\pi\epsilon_0 r^2} \rightarrow \boxed{F = \frac{Q^2}{4\pi\epsilon_0 r^2}}$$

## Example : Surface Charge Density

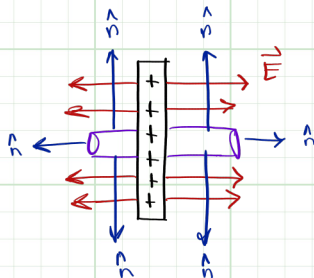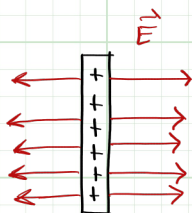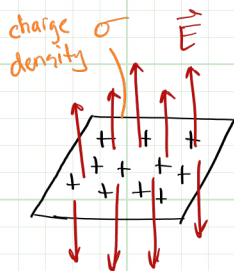

$$\begin{aligned}
 \oiint \vec{E} \cdot d\vec{A} &= \oiint_{\text{left}} \vec{E} \cdot d\vec{A} + \oiint_{\text{right}} \vec{E} \cdot d\vec{A} + \oiint_{\text{side}} \vec{E} \cdot d\vec{A} \\
 &= \oiint_{\text{left}} E \cos(0) dA + \oiint_{\text{right}} E \cos(0) dA + \oiint_{\text{side}} E \cos(90) dA \\
 &= 2E \oiint dA \\
 &= 2EA
 \end{aligned}$$

$$\oiint \vec{E} \cdot d\vec{A} = \frac{Q}{\epsilon_0} \quad \rightarrow \quad 2EA = \frac{Q}{\epsilon_0}$$


$$2EA = \frac{Q}{\epsilon_0}$$

$$|\vec{E}| = E = \frac{\sigma}{2\epsilon_0}$$

electric field  
for charged  
surface  
(sheet of  
charge)



### Example: Line surface density

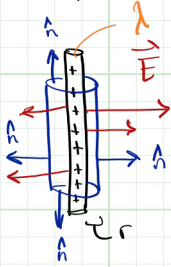

$$\begin{aligned}\oiint \vec{E} \cdot d\vec{A} &= \iint_{\text{top}} \vec{E} \cdot d\vec{A} + \iint_{\text{bottom}} \vec{E} \cdot d\vec{A} + \iint_{\text{side}} \vec{E} \cdot d\vec{A} \\ &= \iint_{\text{top}} E \cos(90) dA + \iint_{\text{bottom}} E \cos(90) dA + \iint_{\text{side}} E \cos(0) dA \\ &= E \iint_{\text{side}} dA = EA = \underline{2\pi r h E}\end{aligned}$$

$$\oiint \vec{E} \cdot d\vec{A} = \frac{Q}{\epsilon_0}$$

$$2\pi r h E = \frac{Q}{\epsilon_0}$$

$$2\pi r \cancel{h} E = \frac{\lambda \cancel{h}}{\epsilon_0}$$

$$E = \frac{\lambda}{2\pi \epsilon_0 r}$$

$$E = \frac{\lambda}{2\pi \epsilon_0 r}$$

← electric field for charged line

### First Shell Theorem

- + a charged particle inside a charged shell experiences no force from the charged shell.
- + this means that there is zero electric field inside an empty charged shell.

### Proof



$$\oiint \vec{E} \cdot d\vec{A} = \frac{Q}{\epsilon_0}$$

← we know  $Q=0$  because the shell is empty, which means either area is zero or electric field is zero or angle b.t.  $\hat{n}$  and  $\vec{E}$  is always  $90^\circ$

∴ Only way LHS=RHS is if  $\vec{E}$  is 0


## Second Shell Theorem



- you can take all the amount of charge of the shell and concentrate it at the centre.
- replace shell with point charge  $Q = 4\pi R^2 \sigma$  at centre
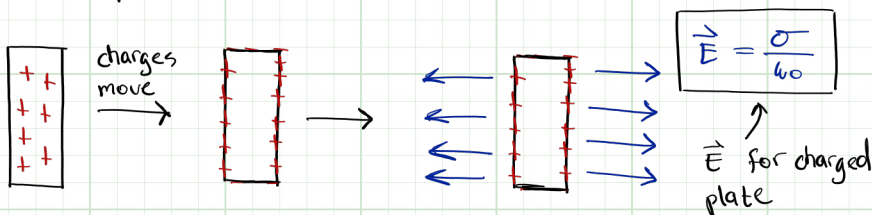
## Charged Plate

- Any charge put inside the perfect metal moves to the surface
- $\vec{E}$  inside perfect metal is zero.



## Things To Know

- Potential Energy : P.E or  $U$  or  $\Delta U \rightarrow$  P.E
- Electrostatic Potential :  $V$  or  $\Delta V$  or Voltage  $\rightarrow$  E.P
- Work Applied :  $W_{app}$ , work done by external agent  $\rightarrow W_{appl}$
- $W_{field}$  : Work done by a field  $\rightarrow W_{field}$

$$U_F - U_i = \Delta U = W_{appl} = -W_{field}$$


\* If work is done by external agent ...

$$\Rightarrow W_{\text{appl}} > 0 \quad \Leftrightarrow W_{\text{field}} < 0$$


\* If work is done by field ...

$$\Rightarrow W_{\text{field}} > 0 \quad \Leftrightarrow W_{\text{appl}} < 0$$

### How This Makes Sense

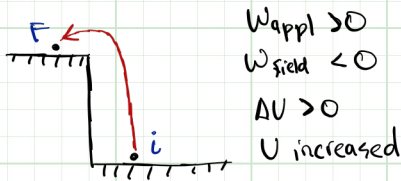

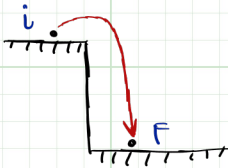
$$\begin{aligned} W_{\text{appl}} &> 0 \\ W_{\text{field}} &< 0 \\ \Delta U &> 0 \\ U &\text{increased} \end{aligned}$$



$$\begin{aligned} W_{\text{field}} &> 0 \\ W_{\text{appl}} &< 0 \\ \Delta U &< 0 \\ U &\text{decrease} \end{aligned}$$

### Electromagnetism

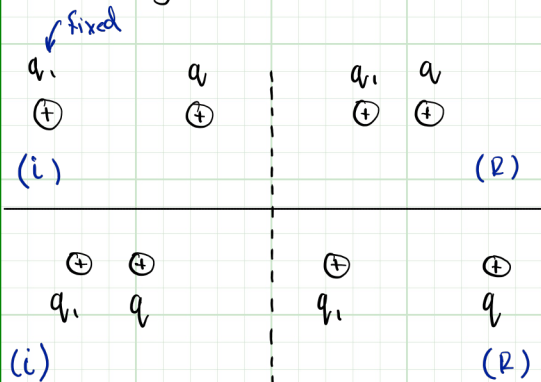


$$\left. \begin{aligned} W_{\text{appl}} &> 0 \\ W_{\text{field}} &< 0 \\ \Delta U &> 0 \end{aligned} \right\} \begin{aligned} &U \text{ increased} \\ &V \text{ increased} \end{aligned}$$

$$\Delta V = \frac{\Delta U}{q} = \frac{(+)}{(+)} > 0$$

$$\left. \begin{aligned} W_{\text{field}} &> 0 \\ W_{\text{appl}} &< 0 \\ \Delta U &< 0 \end{aligned} \right\} \begin{aligned} &U \text{ decreased} \\ &V \text{ decreased} \end{aligned}$$
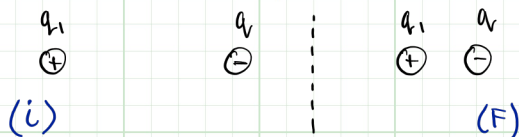
$$\Delta V = \frac{\Delta U}{q} = \frac{(-)}{(+)} < 0$$



$$\left. \begin{array}{l} W_{\text{field}} > 0 \\ W_{\text{app}} < 0 \\ \Delta V < 0 \end{array} \right\} \begin{array}{l} V \text{ decreased} \\ V \text{ positive} \end{array}$$

$$\Delta V = \frac{\Delta U}{q} = \frac{(-)}{(-)} > 0$$

What is Voltage?

$$V_F - V_i = \Delta V = \frac{U_F - U_i}{q} = \frac{\Delta U}{q} = \frac{W_{\text{app}}}{q} = -\frac{W_{\text{field}}}{q}$$

$$\Delta V = \left[ \frac{\text{J}}{\text{C}} \right] = [\text{Volt}] = [V]$$


q enters with algebraic sign

- When a particle moves against the electric field, the change in voltage is positive (voltage increases)
- Charge goes against field = Voltage goes up
- Charge goes along field = Voltage goes down

Equation

$$\Delta V = V_F - V_i = \int_i^F \vec{E} \cdot d\vec{s}$$

# Electrostatic Potential

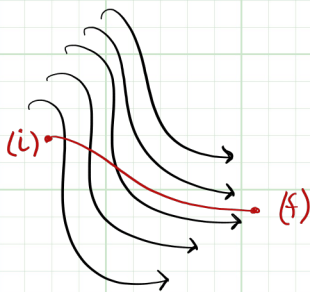

$$V_f - V_i = \Delta V = - \int_i^f \vec{E} \cdot d\vec{s}$$

$$\vec{F} = q\vec{E}$$

$$\Delta V = \frac{-W_{\text{field}}}{q} \Rightarrow W_{\text{field}} = \Delta V(-q)$$

$$W_{\text{field}} = \vec{F} \cdot \vec{s}$$

$$dW_{\text{field}} = \vec{F} \cdot d\vec{s}$$

$$\int dW_{\text{field}} = \int_i^f \vec{F} \cdot d\vec{s}$$

$$W_{\text{field}} = \int_i^f \vec{F} \cdot d\vec{s}$$

$$W_{\text{field}} = q \int_i^f \vec{E} \cdot d\vec{s}$$

$$\Delta V(-q) = q \int_i^f \vec{E} \cdot d\vec{s}$$


$$\Delta V = - \int_i^f \vec{E} \cdot d\vec{s}$$

$$\therefore \Delta V = V_f - V_i = - \int_i^f \vec{E} \cdot d\vec{s}$$

## Example

$$\vec{E} = -|E_0|\hat{j}$$
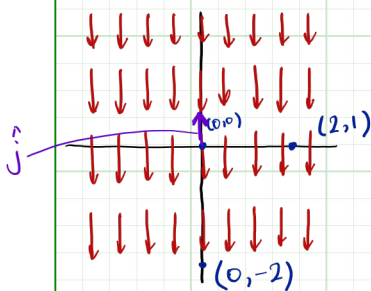
$$d\vec{s} = dx\hat{i} + dy\hat{j} + dz\hat{k}$$



$$V_{(0,-2)} - V_{(0,0)} = - \int_{(0,0)}^{(0,-2)} \vec{E} \cdot d\vec{s}$$

$$= - \int_{0,0}^{0,-2} |\vec{E}| \cos 180^\circ |\vec{E}| ds$$

$$= -|E_0| \cos 180^\circ \int_{0,0}^{0,-2} dy$$

$$= -|E_0| \cos 180^\circ \left[ y \right]_0^{-2}$$

$$= -2|E_0|$$

## 2nd Method


$$V_{0,0} - V_{0,-2} = \Delta V$$

$$= - \int_{y=0}^{y=-2} |E_0| \hat{j} \cdot d\mathbf{y} \hat{j} = |E_0| \int_{y=0}^{y=-2} dy = -2|E_0|$$

Part B = Move to (0,2) and then to (0,-2)

$$(1) V_{2,0} - V_{0,0} = - \int_{0,0}^{2,0} |E_0| \cos \angle \hat{j} \cdot d\mathbf{s} \quad \cos(90^\circ) = 0$$

$$V_{2,0} - V_{0,0} = - \int_{0,0}^{2,0} -|E_0| \hat{j} \cdot d\mathbf{x} \hat{i} \quad \hat{j} \cdot \hat{i} = 0$$

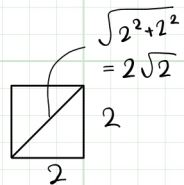


$$(2) V_{0,-2} - V_{2,0} = - \int_{2,0}^{0,-2} -|E_0| \cos \angle \hat{j} \cdot d\mathbf{s} \quad \cos(45^\circ) = \frac{1}{\sqrt{2}}$$

$$= -|E_0| \frac{1}{\sqrt{2}} \cdot 2\sqrt{2} = -2|E_0|$$


$$V_{0,-2} - V_{2,0} = - \int_{0,2}^{0,-2} |E_0| \hat{j} \cdot [d\mathbf{x} \hat{i} + d\mathbf{y} \hat{j}] \quad \begin{aligned} \hat{j} \cdot \hat{i} &= 0 \\ \hat{j} \cdot \hat{j} &= 1 \end{aligned}$$
$$= |E_0| \int_{y=0}^{y=-2} dy = -2|E_0|$$

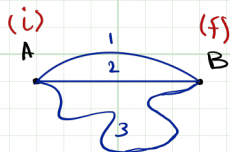\* Electrostatic field is conservative field



It doesn't matter what path you take  
Voltage depends only in  $\Delta V = V_f - V_i$

### Voltage of Point Charge at Distance

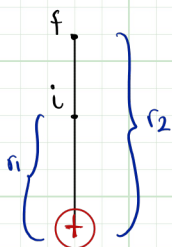

$$\Delta V = V_f - V_i = V_{r_2} - V_{r_1}$$

$$= - \int_{r=r_1}^{r=r_2} \vec{E} \cdot d\vec{s}$$

$$\cos(0) = 1$$

$$= - \int |\vec{E}| ds \cos \angle \vec{E} \cdot d\vec{s}$$

$$= - \int_{r=r_1}^{r=r_2} \frac{q}{4\pi\epsilon_0 r^2} dr$$

$$= - \frac{q}{4\pi\epsilon_0} \left( -\frac{1}{r} \right)_{r=r_1}^{r=r_2}$$


$$V_{r_2} - V_{r_1} = \frac{q}{4\pi\epsilon_0} \left( \frac{1}{r_2} - \frac{1}{r_1} \right)$$

Now let  $r_2 \rightarrow \infty$ ,  $V_{r_2} = 0$

$$-V_{r_1} = -\frac{q}{4\pi\epsilon_0 r_1} \Rightarrow$$


$$V_q(r) = \frac{q}{4\pi\epsilon_0 r}$$

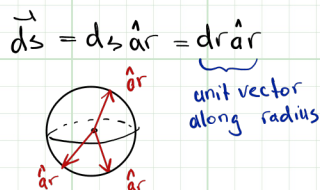↙ Voltage of signed point charge  $q$  at a distance  $r$  from charge



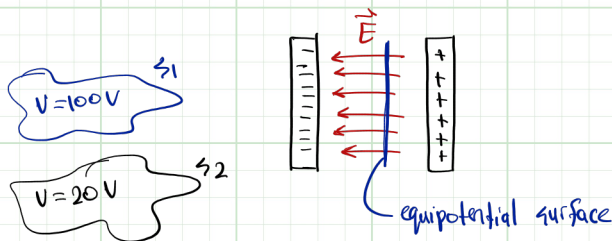
## Equipotential Surfaces

- + a surface where voltage is the same anywhere on it.
- voltage doesn't change when moving on field
- + Electric field is  $\perp$  everywhere to equipotential surface


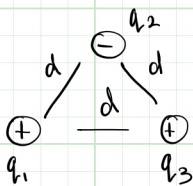
## Electric Potential Energy of System

- + The total potential energy of a system of particles is the sum of the potential energies for every pair of particles in the system



$$U = U_{1,2} + U_{1,3} + U_{2,3}$$

$$= \frac{1}{4\pi\epsilon_0} \left( \frac{q_1 q_2}{d} + \frac{q_1 q_3}{d} + \frac{q_2 q_3}{d} \right)$$


$q$  enters with algebraic sign

$$U = \frac{q_1 q_2}{4\pi\epsilon_0 r}$$

electric potential energy of 2 charge system



# Capacitors and Capacitance

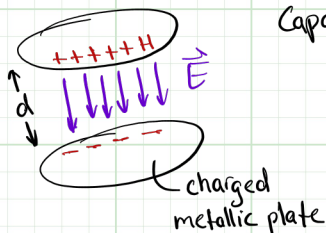

Capacitance

$$C = \frac{Q}{V}$$

absolute value  
of charge on  
one plate



capacitance  
(always +)

$\Delta V$ : voltage diff  
btwn 2 plates

\* units for capacitance  $C$  is  $= \frac{[C]}{[V]} = \text{Farad} = F$

\* used to store electric energy

## Parallel Plate Capacitor

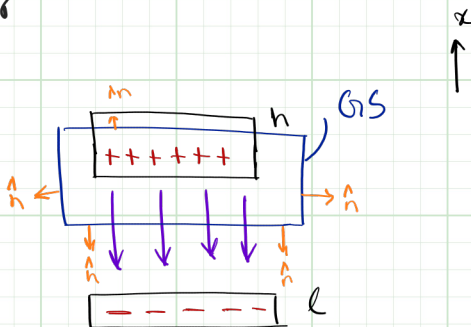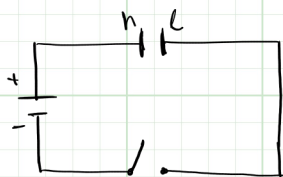

$$\oint_{\text{GS}} \vec{E} \cdot d\vec{A} = \frac{Q_{\text{enc}}}{\epsilon_0} \Rightarrow \int E dA \cos \angle \hat{E} \cdot \hat{n} = \frac{Q_{\text{enc}}}{\epsilon_0}$$

bottom  
surface

$$E = \frac{Q}{\epsilon_0 A}$$

electric field  
of capacitor

area of bottom  
surface

$$E A = \frac{Q}{\epsilon_0} \Rightarrow E = \frac{Q_{\text{enc}}}{\epsilon_0 A}$$

$$\Delta V = - \int_{x=0}^{x=d} \vec{E} \cdot d\vec{s} = - \int_{x=0}^{x=d} E ds \cos \angle \vec{E}, d\vec{s} = - \int_{x=0}^{x=d} \frac{Q}{\epsilon_0 A} \cos(180) dx$$

$$= \frac{Q}{\epsilon_0 A} \int_{x=0}^{x=d} dx = \frac{Qd}{\epsilon_0 A} \quad \boxed{\Delta V = \frac{Qd}{\epsilon_0 A}}$$

$$\Delta V = \frac{Qd}{\epsilon_0 A} \Rightarrow \frac{\epsilon_0 A}{d} = \frac{Q}{\Delta V} \quad \left. \vphantom{\frac{Q}{\Delta V}} \right\} \text{capacitance}$$

↙ area of plate analyzed

$$\boxed{C_{11} = \frac{Q}{V} = \frac{\epsilon_0 A}{d}}$$


capacitance of parallel charged plates

$$\boxed{V = Ed}$$

↖ distance bt 2 plates

• electric field unit  $E = \frac{[V]}{[m]} = \frac{[N]}{[C]}$

## Cylindrical Capacitor

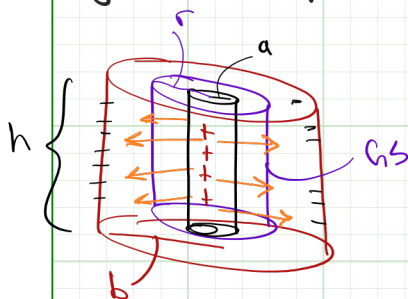

$$\oint_{\text{side}} \vec{E} \cdot d\vec{A} = \iint_{\text{side}} E dA \cos(0) = \frac{Q_{\text{enc}}}{\epsilon_0}$$

$$\boxed{E = \frac{Q_{\text{enc}}}{2\pi\epsilon_0 b h}}$$

Electric field for cylindrical capacitor radius

$$\boxed{V = \frac{Q}{2\pi\epsilon_0 h} \ln\left(\frac{b}{a}\right)}$$


$$\boxed{C = \frac{Q}{V} = \frac{2\pi\epsilon_0 h}{\ln(b/a)}}$$

capacitance of cylindrical capac. of height  $h$  and outer radius  $b$  and inner radius  $a$ .

$$\boxed{C = \frac{C}{h} = \frac{2\pi\epsilon_0}{\ln(b/a)}}$$

capacitance of cylindrical capacitor per unit length

## Spherical Capacitor

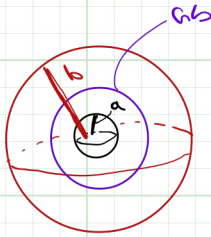

$$C = \frac{Q}{V} = 4\pi\epsilon_0 \cdot \frac{ab}{b-a}$$

Capacitance  
of spherical  
capacitor

## Isolated Spherical Capacitor


$$C = 4\pi\epsilon_0 R$$

$R$  is radius of  
spherical conductor

## Parallel Capacitors

Voltage same across each element

$$Q = VC$$

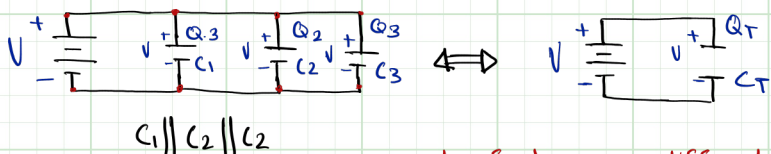


amount of charge is different

$$C_T = C_1 + C_2 + C_3$$

## Series Capacitors

Q current is same

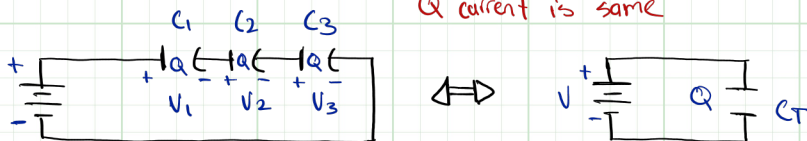


$$C_1 \leftrightarrow C_2 \leftrightarrow C_3$$

$$\frac{1}{C_T} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

or

$$C_T = \left( \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \right)^{-1}$$

## Example

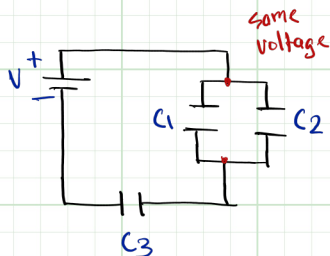


$$C_1 \parallel C_2 = C_1 + C_2$$

$$(C_1 + C_2) \leftrightarrow C_3$$

$$\frac{1}{C_T} = \frac{1}{C_3} + \frac{1}{C_1 + C_2}$$

# Example

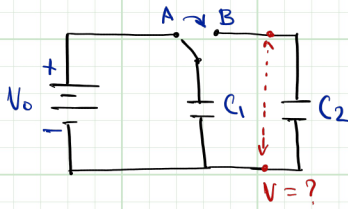


$$Q_0 = C_1 V_0 \quad \text{--- config A}$$

$$Q_0 = C_1 V + C_2 V \quad \text{--- config B}$$

$$C_1 V_0 = V (C_1 + C_2)$$


$$V = \frac{C_1 V_0}{C_1 + C_2}$$

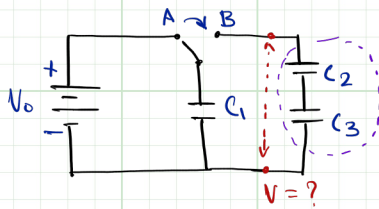the  $Q$  must remain same, so  
to find new voltage, we use  
 $Q_0$  from config A to find  $V$



$$C_T = \frac{1}{C_2} + \frac{1}{C_3}$$

$$C_T = \frac{C_2 C_3}{C_2 + C_3}$$

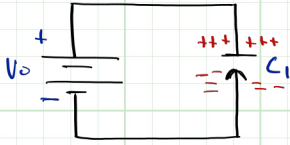Capacitor Storage $\mathcal{U}$ 


$$q = C V$$

$$\Delta \mathcal{U} = q \Delta V$$

$$d\mathcal{U} = q dV$$

energy stored in capacitor
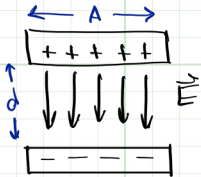
$$\mathcal{U} = \int d\mathcal{U} = \int q dV = \int C' V dV = \frac{1}{2} C V^2 = \frac{1}{2} \frac{q^2}{C} = \frac{1}{2} q V$$



- energy is stored in the electric field
- what is energy density?

$$\mathcal{U} = \frac{1}{2} C V^2 \Rightarrow \frac{\mathcal{U}}{\text{volume}} = u = \frac{1}{2} \frac{C V^2}{d A} \quad E^2 = |\vec{E}|^2$$

$$\frac{\mathcal{U}}{\text{volume}} = u = \left[ \frac{\text{J}}{\text{cm}^3} \right]$$

$$= \frac{1}{2} \frac{\epsilon_0 A}{d^2 A} E^2 d^2$$

$$= \frac{1}{2} \epsilon_0 E^2$$

$$C = \frac{\epsilon_0 A}{d}$$

$$V = E d$$

$$\boxed{u = \frac{1}{2} \epsilon_0 E^2} \quad \begin{array}{l} \text{energy} \\ \text{density for} \\ \text{parallel plate capacitor} \end{array}$$

- +  $\epsilon_0$  is only for vacuum
- we need to modify equation

## Dielectric Constant


$$\epsilon_0 \rightarrow k \epsilon_0 \equiv \epsilon_r \epsilon_0$$

relative permittivity  
permittivity

dielectric constant

$$k = \epsilon_r \text{ (relative permittivity)}$$

$$\epsilon_r > 1$$

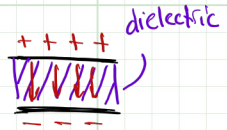

$$F_{2,1} = \frac{1}{4\pi\epsilon_0\epsilon_r} \cdot \frac{q_1 q_2}{r^2}$$


$$C = \frac{\epsilon_0 \epsilon_r A}{d}$$

$$E_{q_1} = \frac{q_1}{4\pi\epsilon_0\epsilon_r r^2}$$

- What happens when we add a dielectric to capacitor?

↳  $C$  increases because  $k = \epsilon_r > 1$

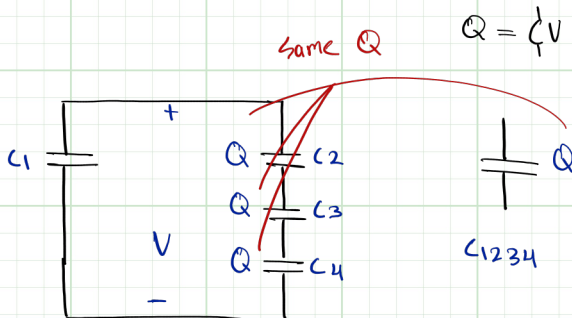- When we remove battery, voltage drops and capacitance increases since  $Q$  must remain constant:  $Q = C V$




# Resistance and Resistors

$$R = \frac{V}{I}$$

resistance of a device
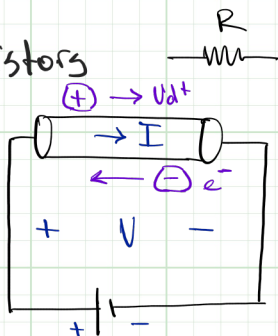
$$R = \left[ \frac{V}{A} \right] = [\Omega]$$



• current is the movement of positive charge

•  $e^-$  move opp

$$I = \frac{dq(t)}{dt}$$

movement of charge is current

$$I = \left[ \frac{C}{s} \right] = [A] \quad \text{one of 7 basic units in SI}$$


$\vec{J}$  current density

by definition

$$\left[ \frac{A}{m^2} \right]$$

only place where density referred as  $m^2$

$$I = \int_A \vec{J} \cdot d\vec{A}$$

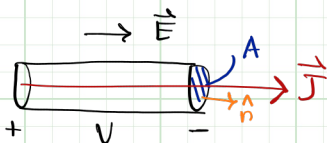

• current is the flux of current density through a surface

Assume  $\vec{J}$  uniform

$$I = \int_A \vec{J} \cdot d\vec{A} = JA$$

$$I = JA$$

current is the current density times area



## Resistance in Micro Scale

- electrons bump into other things and slow down.
- inhibition of electrons is called resistance

$$R = \frac{V}{I} \quad \Leftrightarrow \quad \rho = \frac{|\vec{E}|}{|\vec{J}|} = \frac{E}{J} \Rightarrow \vec{E} = \rho \vec{J}$$

macro scale                      resistivity                      micro scale                       $\frac{1}{\rho} \vec{E} = \vec{J}$

$$\boxed{\rho = \frac{E}{J}} = \left[ \frac{V \cdot m}{A} \right] = [ \Omega \cdot m ]$$

resistivity relates  
resistance to micro scale


$$\boxed{\sigma \vec{E} = \vec{J}}$$

conductivity


$$\sigma = \left[ \frac{1}{\Omega \cdot m} \right]$$

## Expression of Current Density

- drift velocity

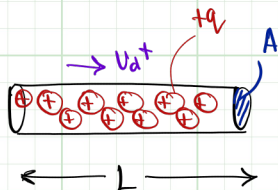

- \* current is movement of charge

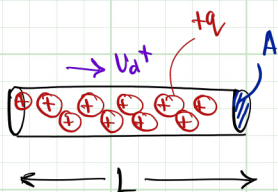

We know  $L = v_d t$

$N$ : density

$$Q = N L A q^+ \quad \leftarrow \text{total charges}$$

$$Q = N v_d t A q^+ \quad \leftarrow \text{total charges in terms of } v_d$$

$$\frac{Q}{t} = N v_d A q^+$$

We know  $\frac{Q}{t} = I$

$$I = N v_d A q^+$$

$$\frac{I}{A} = J^+ = N v_d q^+ \quad \leftarrow \text{current density related to drift density}$$

$$\vec{J}^+ = N \vec{v}_d q^+$$

$$\vec{J}_T = \vec{J}^+ + \vec{J}^- = N^+ \vec{v}_d^+ q^+ + N^- \vec{v}_d^- q^- \quad \leftarrow N^{+ \text{ or } -} \text{ density for (+)ve or (-)ve charges}$$




$$\begin{array}{l} q^+ \quad v_d^+ \\ \oplus \rightarrow \leftarrow \vec{J}^+ = N^+ q^+ \vec{v}_d^+ \quad (N^+) \text{ and } q^+ > 0 \end{array}$$

$$\begin{array}{l} v_d^- \\ \ominus \leftarrow \rightarrow \vec{J}^- = N^- q^- \vec{v}_d^- \quad (N^-) > 0 \text{ but } q^- < 0 \end{array}$$

$$\therefore \vec{J}_T = \vec{J}^+ + \vec{J}^- \longrightarrow \text{same direction}$$

Finding Resistance of Wire
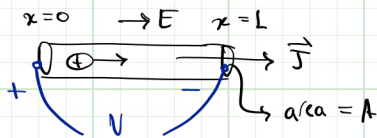
$$R = \rho \frac{L}{A} \quad \leftarrow \begin{array}{l} \text{resistance of } q \\ \text{wire length } L, \text{ cross-sectional} \\ \text{area } A \text{ made of resistivity } \rho \end{array}$$



$$R = \frac{V}{I}$$

$$V = EL$$

$$I = JA$$

$$R = \frac{V}{I} = \frac{EL}{JA} = \rho \frac{L}{A}$$

and since  $\rho = \frac{E}{J}$

## Power Dissipated in Resistor

$$\Delta V = \frac{\Delta U}{q} \Rightarrow q dV = dU$$

$$\int q dV = \int dU$$

we know  $V = IR$

$$\frac{dV}{dI} = R \rightarrow dV = R dI$$

$$\int q R dI = \int dU$$

$$qRI = U$$

$$U = qRI$$

we know rate change of energy  
is given by power

$$P = \frac{\Delta U}{\Delta t}$$

$$\frac{dU}{dt} = \frac{dq}{dt} RI = IRI$$

$$P = I^2 R$$

$P$  is dissipated  
power of a  
resistor

$$P = I^2 R = \frac{V^2}{R} = IV$$

any device ...  
relating  $V$ ,  $I$ , and  
power

$$\text{Power: } [Watt] = [W] = [A \cdot V] \text{ ampere-volt}$$

### Resistors in Parallel

$$I = I_1 + I_2 + I_3 \quad \leftarrow \text{KCL}$$

$$\boxed{\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$

### Resistors in Series

- same current
- different voltage

$$V = V_1 + V_2 + V_3$$

↙ KVL

$$\boxed{R_T = R_1 + R_2 + R_3}$$


### Midterm Review

## Magnetic Field ( $\vec{B}$ )

$$\vec{E} = \frac{\vec{F}}{q} \quad \leftarrow \text{electric force}$$

$\vec{B}$
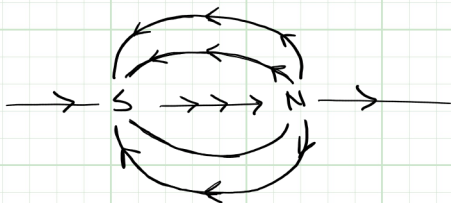
$$\vec{F}_B \quad \leftarrow \text{magnetic force}$$




• magnetic field always starts at North pole and ends at South pole

Magnetic Flux :  $\boxed{\oint \vec{B} \cdot d\vec{A} = 0}$  Gauss Law for magnetic flux

reason why magnetic field lines always loop and close on themselves

- Movement of charge (current) causes magnetic fields.
- Fundamentally, related to magnetic moment (fundamental property of things... like mass, charge etc.)


## Biot - Savart Law

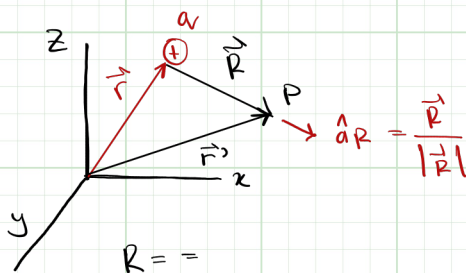

$$\vec{E} = \frac{q}{4\pi\epsilon_0 R^2} \hat{a}_R$$

$$\vec{dB} = \frac{\mu_0 I ds}{4\pi r^2} \times \hat{ar}$$

$$\hat{ar} = \frac{\vec{r}}{|\vec{r}|}$$

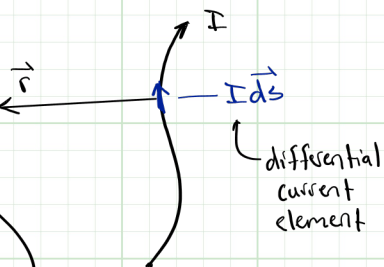

$\mu_0$  permeability of free space


$$\mu_0 = 4\pi \times 10^{-7}$$

Integrate

$$B = \int d\vec{B} = \int \frac{\mu_0 I ds \times \hat{ar}}{4\pi r^2}$$

Biot-Savart Law

Units

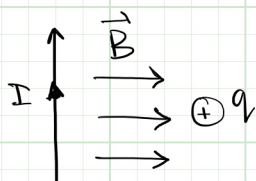


$\vec{F}_B = 0$  if  $q$  doesn't move

$\vec{F}_B = 0$  if  $q$  moves parallel to  $\vec{B}$

$$\boxed{\vec{F}_B = q \vec{v} \times \vec{B}}$$

magnetic force

$$\vec{v} \times \vec{B}$$

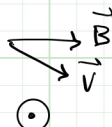

$$\vec{B} = \left[ \frac{N \cdot s}{C \cdot m} \right] = \text{Tesla} = [T] \quad \text{unit for magnetic field } \vec{B}$$


$$= \frac{C \cdot V \cdot s}{m \cdot C \cdot m} = \left[ \frac{V \cdot s}{m^2} \right] = \left[ \frac{\text{Weber}}{m^2} \right]$$

$$\mu_0 = \frac{T \cdot m^2}{A \cdot m} = \left[ \frac{T \cdot m}{A} \right] = \frac{V \cdot s \cdot m}{m^2 \cdot A} = \left[ \frac{V \cdot s}{A} \cdot \frac{1}{m} \right]$$

Henry


$$\mu_0 = \left[ \frac{\text{Henry}}{\text{m}} \right] = \left[ \frac{\text{H}}{\text{m}} \right] \quad \text{unit for } \mu_0 \sim \text{permeability of vacuum}$$

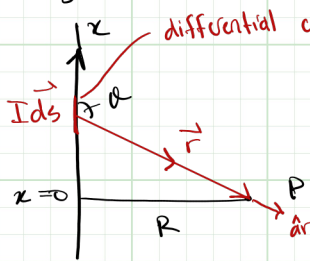Magnetic Field at distance  $r$  from current




$$\vec{B} = \int_{z=-\infty}^{z=\infty} \frac{\mu_0 I ds \times \hat{a}_r}{4\pi r^2}$$

Biot-Savart Law

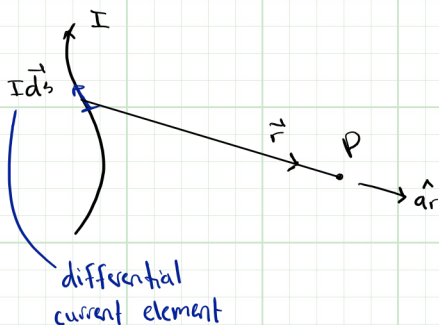

$$\vec{B} = \int \frac{\mu_0}{4\pi r^2} I d\vec{s} \times \hat{a}_r$$

$$\hat{a}_r = \frac{\vec{r}}{|\vec{r}|}$$

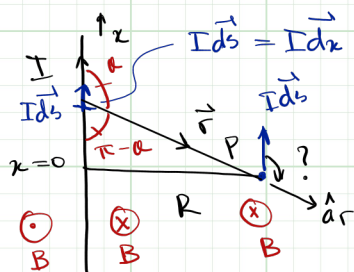

$$\vec{B} = \int_{x=-\infty}^{x=+\infty} \frac{\mu_0 I d\vec{x} \times \hat{a}_r}{4\pi r^2}$$

$$B = \frac{\mu_0}{4\pi} I \int_{-\infty}^{\infty} \frac{dx}{r} \sin\alpha$$

$$\sin\alpha = \sin(\pi - \alpha) = \frac{R}{r}$$

$$r = \sqrt{x^2 + R^2}$$

$$r^3 = (x^2 + R^2)^{3/2}$$

$$B = \frac{\mu_0 I}{4\pi} \int_{-\infty}^{\infty} \frac{dx}{r} \cdot \frac{R}{r}$$

$$= \frac{\mu_0 I R}{4\pi} \int_{-\infty}^{\infty} \frac{dx}{r^3}$$

$$= \frac{\mu_0 I R}{4\pi} \int_{-\infty}^{\infty} \frac{dx R}{(x^2 + R^2)^{3/2}}$$

$$B = \frac{\mu_0 I}{2\pi R} \left[ \frac{x}{\sqrt{x^2 + R^2}} \right]_0^{\infty}$$


$= 1 - 0$

even, so

$$\int_{-\infty}^{\infty} x^2 = 2 \int_0^{\infty} x^2$$


$$B = \frac{\mu_0 I}{2\pi R}$$

magnetic field  
at distance  $R$

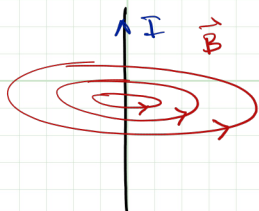



## Less Symmetry Example

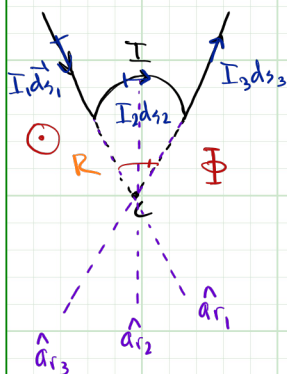

What is  $|\vec{B}|$  at centre C?

$$I_1 = I_2 = I_3$$

$$\vec{dB}_1 \propto I_1 \vec{ds}_1 \times \hat{a}_{r1} = 0 \quad \sin(0) = 0$$

$$\vec{dB}_3 \propto I_3 \vec{ds}_3 \times \hat{a}_{r3} = 0 \quad \sin(180) = 0$$


$$\vec{dB}_2 \propto I_2 \vec{ds}_2 \times \hat{a}_{r2} = 1 \quad \sin(90) = 1$$

$$\vec{B}_2 = \int \frac{\mu_0 I_2 \vec{ds}_2 \times \hat{a}_{r2}}{4\pi R^2}$$

$$\vec{B}_2 = \int_{\Phi}^{\phi=\Phi} \frac{\mu_0 I_2 ds_2}{4\pi R^2} = \int_{\phi=0}^{\phi=\Phi} \frac{\mu_0 I R d\phi}{4\pi R^2} = \frac{\mu_0 I}{4\pi R} \phi \Big|_0^{\Phi}$$

$$\boxed{\vec{B}_2 = \frac{\mu_0 I \Phi}{4\pi R}} \quad \begin{array}{l} \text{magnitude of } \vec{B} \\ \text{at distance } R \text{ and} \\ \text{angle } \Phi \text{ in radian} \end{array}$$

## Magnetic Force Experiment

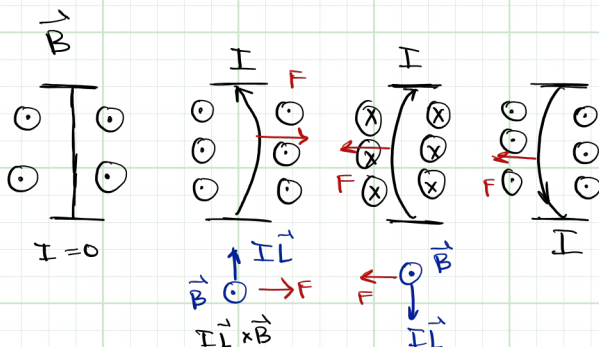

$$\vec{F} = q \vec{v} \times \vec{B}$$

$$d\vec{F} = dq \vec{v} \times \vec{B}$$

$$d\vec{F} = I d\vec{L} \times \vec{B}$$

$$I = \frac{dq}{dt} \Rightarrow dq = I dt$$

$$\vec{v} = \frac{d\vec{L}}{dt}$$


assume wire  
straight, and  
 $\vec{I}$  not dep-  
ending on  
space

$$\vec{F} = \int I d\vec{L} \times \vec{B}$$


$$\boxed{\vec{F}_B = I \vec{L} \times \vec{B}}$$

cross product  
to find  $\vec{F}_B$

Microscopic scale

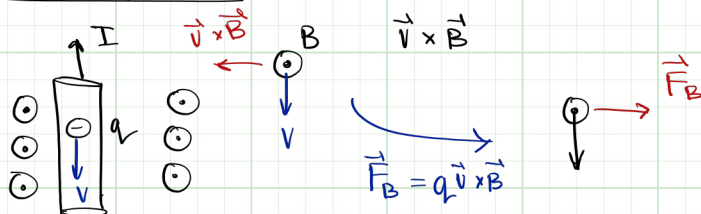

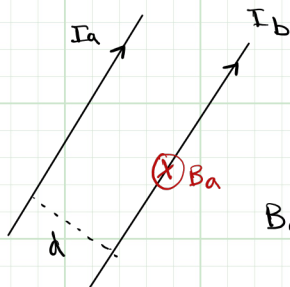the negative  
charge  $q$  switches direction of  $\vec{v} \times \vec{B}$



same direction  $I$ , attracts  
opposite direction  $I$ , repels

$$B_a = \frac{\mu_0 I_a}{2\pi d}$$

$$\vec{F}_{ba} = I_b \vec{L} \times \vec{B}_a$$


$$|\vec{F}_{b,a}| = \frac{\mu_0 L I_a I_b}{2\pi d}$$

Force on wire when it and another wire have current a, b and

distance  $d$  bet. them

- Find the  $\vec{B}$  first, then the  $\vec{F}$
- after finding the  $\vec{B}$  at the wire, use RHR crossing current of the wire you're at (not the other ones) to find the direction of the  $\vec{F}_B$  from each  $\vec{B}$  on the wire you're at.

### Ampere's Law

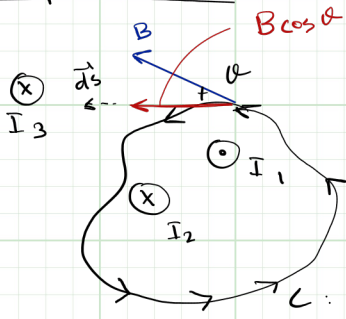

$$\oint_C \vec{B} \cdot d\vec{s} = \mu_0 I_{enc}$$

closed current has algebraic sign

line integral of  $\vec{B}$  over the closed path  $C$  (also called circulation of  $B$ ) is equal to  $\mu_0$  times the current enclosed by  $C$

$$\oint_C \vec{B} \cdot d\vec{s}$$

differential length always tangential

$$\vec{B} \cdot d\vec{s} = B \cos \alpha ds$$

tangential component of  $B$

" tangential component times  $ds$  gives the enclosed current (multiplied by  $\mu_0$ ) "



Ld if Fingers opp. C, I (-)ve }  $\therefore$  in eg. above  
 Ld " " same C, I (+)ve }  $\begin{matrix} I_1 (+)ve \\ I_2 (-)ve \end{matrix}$


## Solenoids

- thumb along direction of current, fingers show  $\vec{B}$  inside coil.
- no  $\vec{B}$  outside solenoid

$$\boxed{B = \mu_0 n I}$$
 magnetic field inside solenoid, where  $n$  is # of wire turn/loops per unit length
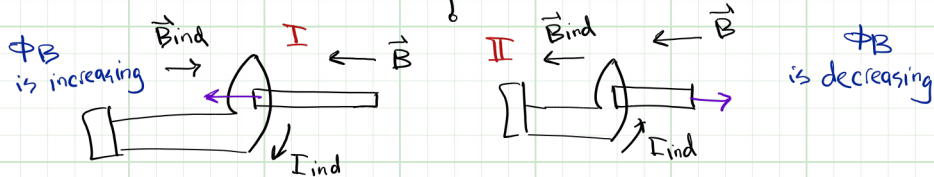
## Faraday Law, Lenz Law

- You'll have current only if there is a  $\Delta$  magnetic flux
- Induced Current ( $I_{ind}$ ): current caused by magnetic field
- EMF: electromotive force



- $I_{ind}$  causes  $\vec{B}_{ind}$
- $\vec{B}_{ind}$  sometimes aids and sometimes hinders  $\vec{B}_{magnet}$

$$\boxed{\oint \vec{E} \cdot d\vec{l} = EMF = -N \frac{d}{dt} \Phi_B = -N \frac{d}{dt} \iint \vec{B} \cdot d\vec{A}}$$

$I_{ind}$  and EMF opposes  $\Delta \Phi_B$       number of loops in coil      time derivative of magnetic flux

- $I_{ind}$  opposes the change in magnetic flux
  - ↳ **I**:  $\Phi_B$  is increasing,  $I_{ind}$  is (-)ve
  - ↳ **II**:  $\Phi_B$  is decreasing,  $I_{ind}$  is (+)ve

### EMF (9.3)

- $EMF = -\frac{d}{dt} \iint \vec{B} \cdot d\vec{A}$
- Unit for EMF is volts (it's a kind of voltage)
- EMF created even if the wire doesn't exist, since EMF only depends on change in magnetic flux.
- EMF is "induced electric field"

$$\mathcal{E} = \oint_c \vec{E} \cdot d\vec{s} \quad \text{v.s.} \quad \Delta V = - \int_i^R \vec{E} \cdot d\vec{s}$$

over a closed loop


- EMF is not the same as a regular voltage (in electrostatics)
- You can change flux by changing angle b.t.  $\vec{B}$  and  $d\vec{A}$

For Electrostatic Voltage

$$\Delta V = - \int \vec{E} \cdot d\vec{s} \longrightarrow \oint \vec{E} \cdot d\vec{s} = 0$$


But for EMF
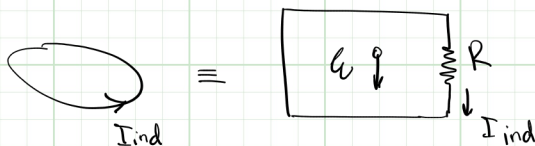
$$\mathcal{E} = \oint \vec{E} \cdot d\vec{s} = -\frac{d}{dt} \Phi_B = -\frac{d}{dt} \iint \vec{B} \cdot d\vec{A} \longrightarrow \text{can't be zero}$$


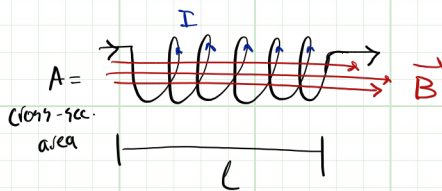
# Inductance

- inductance of inductor
- self induction
- energy stored in inductor
- Voltage across an inductor
- $\parallel$  and  $\leftrightarrow$  connection
- solenoid  $\equiv$  inductor
- stores magnetic energy




$N \triangleq$  total # of loops

$n \triangleq$  number of loops per unit length  $[1/\text{cm}]$

$$\therefore n = \frac{N}{l} \Rightarrow N = nl$$

## Inductance

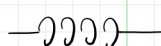  $B = \mu_0 n I \Rightarrow \Phi_B = BA = \mu_0 n I A$

inductance definition

$N\Phi_B$  called magnetic flux linkage

$$L = \frac{N\Phi_B}{I} = \frac{N\mu_0 n \cancel{I} A}{\cancel{I}} = nL\mu_0 n A = n^2 A l \mu_0$$


$$L = n^2 A l \mu_0$$

inductance for inductor length  $l$ ,  
 $n$  is # loops/unit length  
and cross-sec. Area  $A$ .


$$L = \left[ \frac{1}{\text{m}} \cdot \text{m}^2 \cdot \frac{\text{H}}{\text{m}} \right] = [\text{H}]$$

henry

## Self Induction

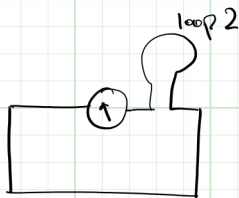

$$\mathcal{E} = -\frac{d}{dt} N\Phi_B$$

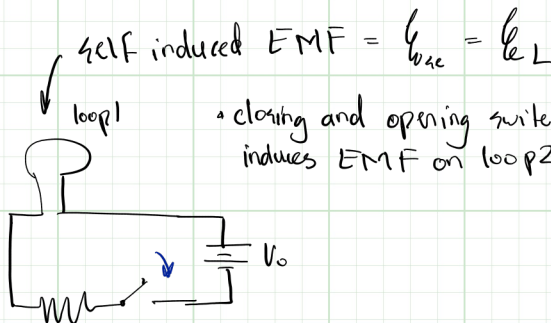


• closing and opening switch induces EMF on loop 2


- When you close the switch, current starts flowing through loop 1.  
 $\hookrightarrow \Delta \Phi_B$  penetrates loop 2, causing  $\oint$  EMF
- The  $I_{ind}$  in loop 2 causes another  $I_{ind}$  / EMF in loop 1  
 $\hookrightarrow$  call this self induced EMF

$$\text{self induction} = \oint_{\text{induced}} = \oint \mathcal{E}_L = -\frac{d}{dt} N \Phi_B$$

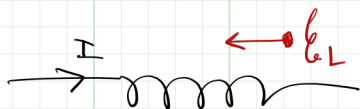- $\mathcal{E}_L$  opposes the change in loop 1 itself.




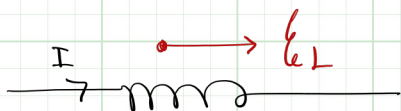$I$  is increasing  
 $B$  is increasing  
 $\Phi_B$  is increasing  
 $\mathcal{E}_L$  opposes current



$I$  is decreasing  
 $B$  is decreasing  
 $\Phi_B$  is decreasing  
 $\mathcal{E}_L$  aids current

### Circuits

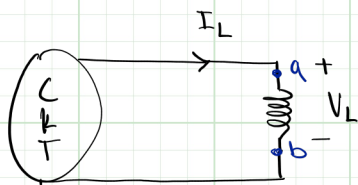

- can't do voltage inside inductor

Find expression for  $V_L$

$$V_L = L \frac{dI_L}{dt} \quad [H] = \left[ \frac{V \cdot s}{A} \right]$$



$$L = \frac{N\Phi_B}{I}, \text{ also } \mathcal{E}_L = -\frac{d}{dt} N\Phi_B$$

$$N\Phi_B = LI$$

• inductance depends on geometry

$$\text{so } \mathcal{E}_L = -\frac{d}{dt} LI = -L \frac{dI}{dt}$$


inductance  $\rightarrow$  assuming time doesn't affect

$$\mathcal{E}_L = -L \frac{dI_L}{dt}$$


$$V_L = -\mathcal{E}_L = L \frac{dI}{dt}$$

Voltage across inductor with inductance  $L$

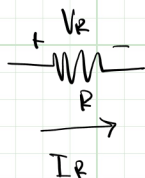- Inductor is differentiator for current
- Integrate  $V_L$  to get charge



$$V_R = I_R R$$

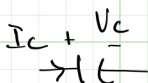


$$Q = C V_C$$

$$\frac{dQ}{dt} = C \frac{dV_C}{dt}$$

$$I_C = C \frac{dV_C}{dt}$$

Open to DC  
no current

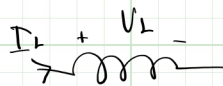

$$V_L = L \frac{dI_L}{dt}$$

↳ "short" to DC  
no voltage

### Inductor Energy Storage

$$dU = dq V$$

$$dU = I dt V$$

$$dU = I \cancel{dt} L \frac{dI}{\cancel{dt}}$$

$$I = \frac{dq}{dt} \quad dq = I dt$$


$$\int dU = \int I L dI$$

$$U = \frac{1}{2} L I^2$$


energy stored in inductor with current  $I$  and inductance  $L$

Series current same
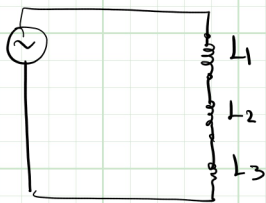
$$V = V_1 + V_2 + V_3 \quad (\text{KVL})$$




$\equiv$

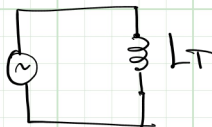


$$L_T = L_1 + L_2 + L_3$$

Parallel voltage same

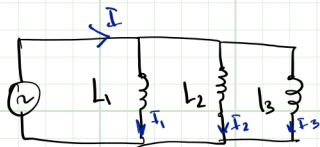

$\equiv$

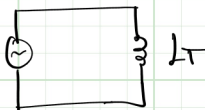

$$I = I_1 + I_2 + I_3 \quad (\text{KCL})$$

$$L_T = \left( \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} \right)^{-1}$$

—mm—

$$V_L = L \frac{dI}{dt} \leftarrow \text{if } \frac{dI}{dt} = 0, V_L = 0, \text{ so short } \circ - \circ$$

—|<—

$$I_C = C \frac{dV_C}{dt} \leftarrow \text{if } \frac{dV_C}{dt} = 0, I_C = 0, \text{ so open } - \circ \quad \circ -$$


——

$$V_R = R I_R$$

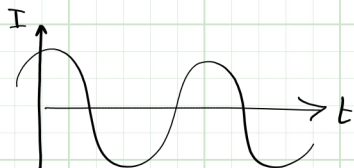
### Applications

$$\mathcal{E}_L = -N \frac{d}{dt} \Phi_B = -N \frac{d}{dt} \iint_S \vec{B} \cdot d\vec{A}$$

- either increase area or
- change angle  $\rightarrow$  generator loop rotating
- in generator, angle bt coil and  $\vec{B}$  changes sinusoidally, so does voltage as a result



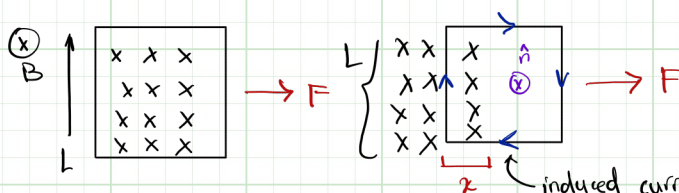Mechanical  $\rightarrow$  Electrical assume  $v$  is constant (no  $a$ )



- area is changing with time
- the induced  $\vec{B}$  must aid the original  $\vec{B}$ , so the  $\vec{B}_{ind}$  should go into page and  $\therefore I_{ind}$  is clockwise

$$|\mathcal{E}| = \left| -\frac{d}{dt}(B \times L) \right| = \left| BL \frac{dx}{dt} \right| = BLv$$

$$|I_{ind}| = \frac{|\mathcal{E}|}{R} = \frac{BLv}{R}$$

$I_{ind}$  with  $B$  and  $L$  and velocity,  $R$  resistance

since  $\mathcal{E} = IR$



model as



$$\text{recall } P = I^2 R$$


$$P_{diss} = I_{ind}^2 R$$

$$P_{diss} = \frac{B^2 L^2 v^2}{R}$$

power dissipation with  $B$ ,  $L$ , and velocity  $v$

$$\frac{dw}{dt} = P = \vec{F} \cdot \frac{d\vec{x}}{dt} = \vec{F} \cdot \vec{v}$$

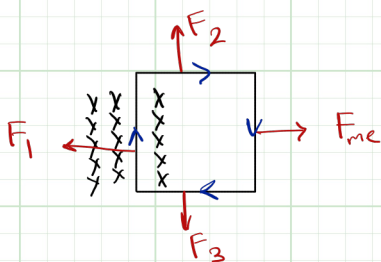work related to power, force and velocity.



since we said no  $\vec{a}$ ,

$$F_{net} = 0$$

$$F_1 + F_2 + F_3 + F_{me} = 0$$

\*  $F_2$  and  $F_3$  cancel each other out up  $\leftrightarrow$  down.

so  $|F_{\text{net}}| = |F_1|$

I know what  $|F_1|$  is since it's a current-carrying wire going through  $\vec{B}$ , so  $|F_1| = I \vec{L} \times \vec{B}$ , and we know angle =  $90^\circ$   
 $\sin(90) = 1$

$$F_1 = I_{\text{ind}} L \times B$$

$$\therefore F_1 = F_{\text{net}} = \frac{B^2 L^2 v}{R}$$

$$P = \vec{F} \cdot \vec{v} = Fv \cos(0) = Fv$$

## Eddy Currents

magnetic fields induced when change in magnetic flux induces current called eddy currents (messy whirlpools).

Figure shows a rectangular wire loop of total resistance  $R$  of dimensions  $H$  and  $L$  placed inside a non-uniform time varying magnetic field given by  $\vec{B} = A_0 x \sin(\omega t) \hat{k}$ , where  $A_0$  and  $\omega$  are positive constants.


a) What is the direction of EMF (clockwise or counterclockwise) induced in the wire for  $0 < \omega t < \pi/2$ . Justify your answer. [2Pts]

b) What is the magnitude of the EMF as a function of  $H$  and  $L$  (and other parameters) for all times? [4Pts]


c) What is the magnitude of the induced current as a function of  $H$  and  $L$  (and other parameters) for all times? [2Pts]

d) How much power is dissipated in the wire? [2Pts]

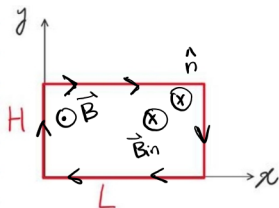e) Who or what is proving the dissipated power? {Shall I ask this question ?}



a)

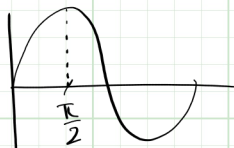

must be into page and

For  $0 < \omega t < \frac{\pi}{2}$ , sin function is increasing, meaning  $\Phi_B$  increases  
To oppose the increasing  $\Phi_B$ ,  $\vec{B}_{ind}$

$\therefore$  direction of EMF is CW

$$b) \Phi_B = \iint A_0 x \sin \omega t \, dx \, dy \cos(180)$$

$$= -A \sin \omega t \int_0^L x \, dx \int_0^H dy$$

$$= -A \sin \omega t \left( \frac{x^2}{2} \right)_0^L (y)_0^H$$


$$= -A \sin \omega t \frac{L^2}{2} H$$

$$|w| = \left| -\frac{d}{dt} \Phi_B \right| = \left| \frac{d}{dt} \left( A_0 \sin \omega t \frac{L^2}{2} H \right) \right| = \frac{A_0 L^2 H \omega}{2} |\cos \omega t|$$

c)  $|I_{ind}| = \frac{|w|}{R} = \frac{A_0 L^2 H \omega |\cos \omega t|}{2R}$

d)  $P_{diss} =$

Figure shows a metallic wire loop in the shape of an equilateral triangle (all sides are equal having the length  $a$  centimeter) immersed in a magnetic field  $\vec{B}$ . The magnetic field ( $\vec{B}$ ) is uniform in space, pointing into the page, but changes with time according to  $t e^{-t}$  (T). Considering the time interval  $0 < t < 1$  second, answer the following questions.

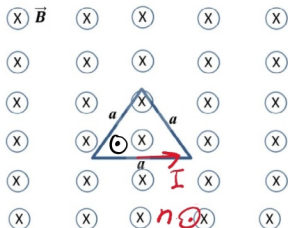


a) Derive an expression for the magnitude of the induced current in terms of  $a$  and  $t$ , assuming each side of the triangle has a resistance  $R$  ( $\Omega$ ). What is the direction of the induced current (clockwise or counter clockwise)? [6 Pts]

b) Obtain an expression for the total power dissipated in the metallic loop. Show all your work. (Try to simplify your answer as much as possible). [2Pts]

c) Suppose that each side of the triangle is doubled in length, while the loop is still entirely immersed in the magnetic field. As compared to the part (a), does the induced current increase or decrease and by how much? Show all your work. [2Pts]

a)  $B(t) = t e^{-t}$

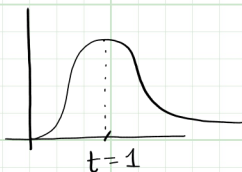

For  $0 < t < 1$ ,  $\vec{B}$  is increasing, so  $I_{ind}$  must be CCW so that  $B_{ind}$  opposes  $\Delta \Phi_B$

$$|\mathcal{E}| = \left| -\frac{d}{dt} \Phi_B \right|$$

$$\Phi_B = \iint t e^{-t} dA \cos 180^\circ = -t e^{-t} A \quad \rightarrow A = \frac{\sqrt{3} a^2}{4}$$


$$\Phi_B = -t e^{-t} \frac{\sqrt{3} a^2}{4}$$

$$|\mathcal{E}| = \left| -\frac{d}{dt} \Phi_B \right| = \frac{d}{dt} \left( -t e^{-t} \frac{\sqrt{3} a^2}{4} \right) = \frac{a^2}{4\sqrt{3}R} (1 - t e^{-t})$$

$$I_{ind} = \frac{|\mathcal{E}|}{R} =$$




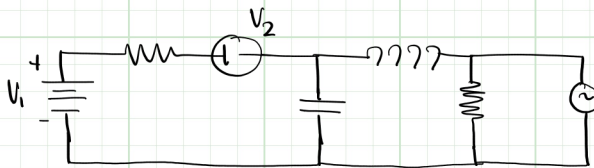
- Solving ckt  $\rightarrow$  find  $V$  and  $I$  for every element




- ckt: collection of electrical elements, lets charges move  
provides path for current  
does info processing

### Current in Ckt


- can be (+) and (-)

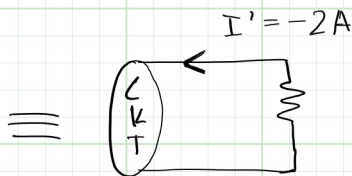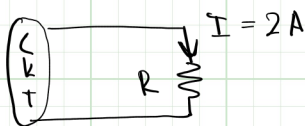

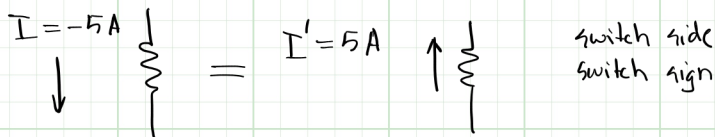- current shows movement of (+)ve charges




### Voltage in Ckt

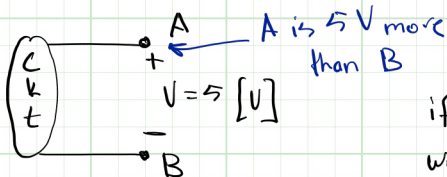

if  $A = 5$   $A = 0$   $A = -5$   
 $B = 0$   $B = -5$   $A = -10$


if 1 C moves  $A \rightarrow B$ ,  
 we will lose 5J of energy

## Changing polarity

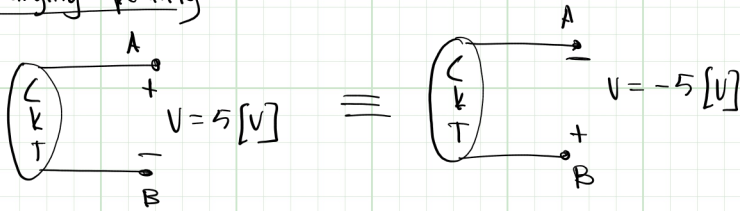

switch polarity, switch sign

## Equivalent Ckts

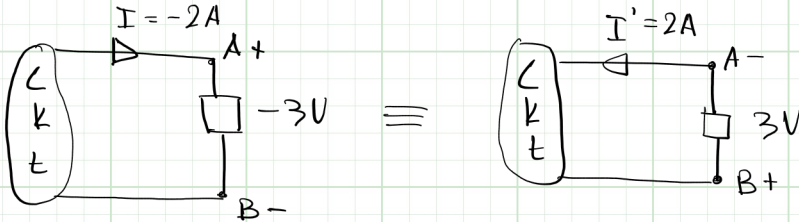


## Convention for Power

$$P = IV$$

"dissipated power is (+)"

if element dissipates power, power is (+)

if element supplies power, power is (-)

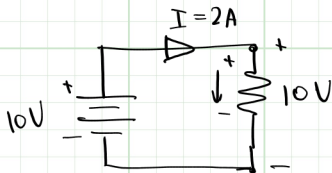


dissipated power  $> 0$

supplied power  $< 0$

- \* if positive current enters (+) terminal of element, that power must be dissipated, or (+)

- \* if positive current leaves the (+) terminal, that power is supplied, or (-)

Eg:

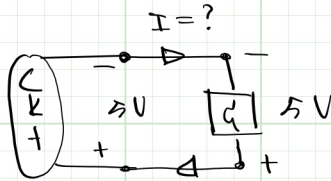

$$P_L = +40 \text{ [W]}$$


$$|I| = \frac{|P|}{|V|} = \frac{40}{5} = 8$$

since (+) current leaves (+) element, so power is supplied, so it's negative

$$\therefore I = -8 \text{ A}$$

## Voltage Source



- \* independent Voltage source:

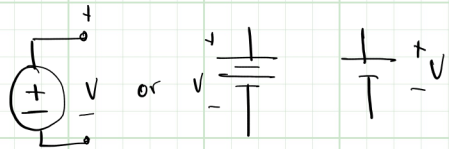


ideal " gives us same voltage no matter how many elements we add or how much current we draw from it

- \* dependent Voltage source:

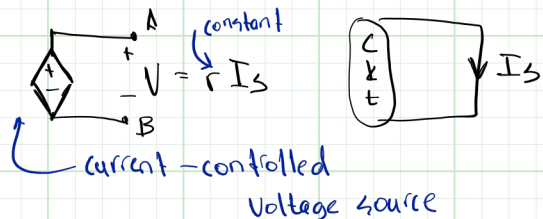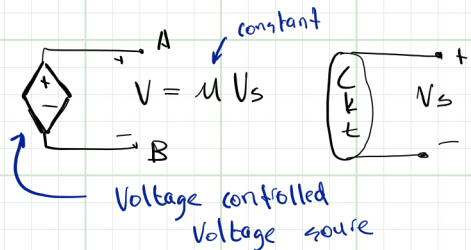voltage can either depend on the current somewhere else or voltage elsewhere



Eg:

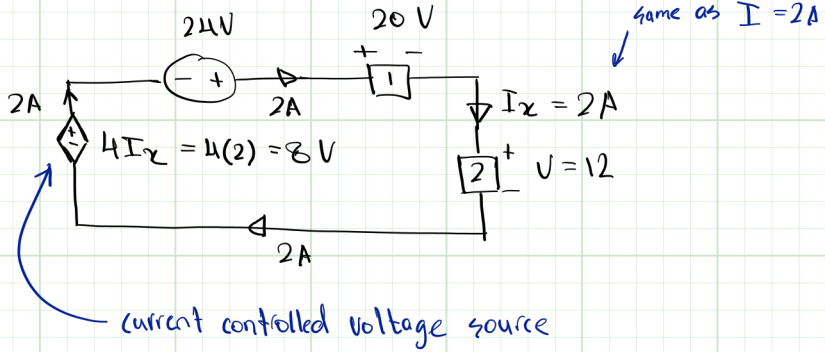

Power in  $\begin{matrix} - & + \\ \text{---} & \text{---} \end{matrix} 24V$

$$|P| = IV = 2 \times 24 = 48 \text{ W}$$

since (+) current leaves (+) terminal, power is (-) and supplied or enters (-)

$$P_{24} = -48 \text{ [W]}$$

Power in  $\begin{matrix} + & - \\ \boxed{1} & \text{---} \end{matrix} 20V$

$$|P| = IV = 2 \times 20 = 40$$

(+) I enters (+) terminal, so power is (+) and  $\therefore$  dissipated

$$\therefore P_1 = +40 \text{ [W]}$$

Power in  $\begin{matrix} + & - \\ \boxed{2} & \text{---} \end{matrix} V = 12$

$$|P| = IV = 2 \times 12 \quad P_2 = 24 \text{ [W]}$$


Power in  $\begin{matrix} + \\ \text{---} \\ - \end{matrix} V = 8V$

$$|P| = 2 \times 8 = 16$$

$$P = -16 \text{ [W]}$$

## Current Sources

### Independent Current Source

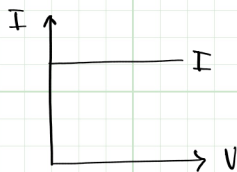

Provides constant



### Dependent Current Source

↳ Voltage-controlled current source

$$I = g V_s$$


↳ current-controlled current source

$$I = \beta i_s$$



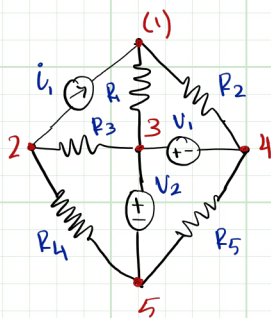
## Nodes, Branches, Loops

\* **node**: a point in a circuit where 2 or elements come together



$\equiv$

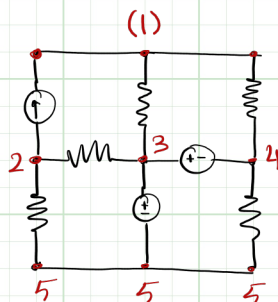


\* **Branch**: a part of a circuit that contains an element.

\* **Loop**: a closed path, you start somewhere and end up the same place without visiting a node more than once
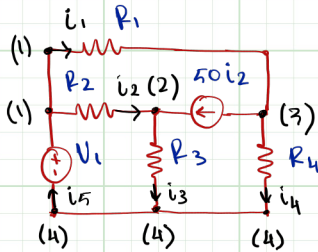
## Kirchoff Current Law

- \* algebraic sum of the current of each node is 0.
- \* for each node in ckt, **current entering = current leaving**



- \* enter  $i$  values w/h algebraic sign
- \* 4 equations, but one of them is extra


Node 1:  $i_5 = i_1 + i_2$

Node 2:  $i_2 + 50i_2 = i_3$

Node 3:  $i_1 = 50i_3 + i_4$

Node 4:  $i_3 + i_4 = i_5$

## Applying KCL to a closed surface

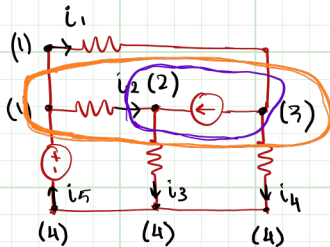


Surface:  $i_2 + i_1 = i_3 + i_4$   
Purple

Orange:  $i_5 + \cancel{i_1} = i_3 + i_4 + \cancel{i_1}$   
 $i_5 = i_3 + i_4$

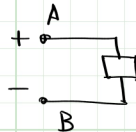
## Kirchoff Voltage Law

- \* algebraic sum of voltages along loop is zero.
- \* Potential Drop/Decrease:  $A \rightarrow B$
- \* Potential Rise/Increase:  $B \rightarrow A$



- \* As u go around loop,

**potential increase = potential decrease**

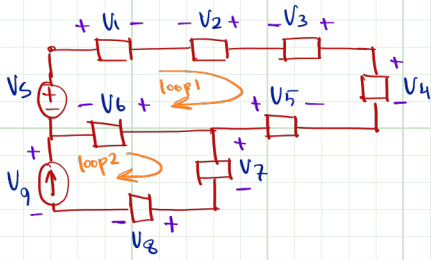

Loop 1


$$V_2 + V_3 + V_5 + V_6 = V_1 + V_4 + V_6$$

Loop 2

$$V_6 + V_9 = V_7 + V_8$$

\* enter values where they are with their algebraic sign.

## Example Ckt

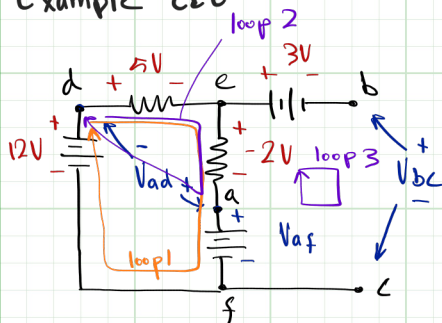

Loop 1

$$PI = PD$$

$$12 = 5 - 2 - V_{af}$$

$$V_{af} = 9V$$

Loop 2

$$PI = PD$$

$$0 = 5 - 2 + V_{ad}$$

$$V_{ad} = -3V$$

Loop 4

$$PI = PD$$

$$V_{af} - 2 = 3 + V_{bc}$$


$$V_{bc} = V_{af} - 2 - 3$$

$$= 9 - 2 - 3$$

$$V_{bc} = 4V$$

Note that point c and f are the same node since they have no elements between them.

## Voltage Divider Ckt

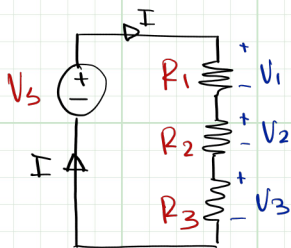

$$PI = PD$$

$$V_s = V_1 + V_2 + V_3$$

$$V_s = IR_1 + IR_2 + IR_3$$

$$V_s = I(R_1 + R_2 + R_3)$$

$$I = \frac{V_s}{R_1 + R_2 + R_3}$$

← got current, can find  $V_1, V_2, V_3$

$$\therefore V_1 = IR_1 = \frac{V_s R_1}{R_1 + R_2 + R_3}$$

$$V_2 = IR_2 = \frac{V_s R_2}{R_1 + R_2 + R_3}$$


$$V_3 = IR_3 = \frac{V_s R_3}{R_1 + R_2 + R_3}$$

$$V_k = V_s \cdot \frac{R_k}{\sum_{j=1}^n R_j}$$

← source voltage



## Current Divider Ckt

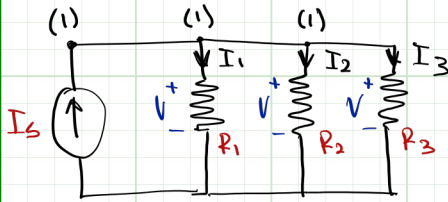

$$CE = CL$$

$$I_s = I_1 + I_2 + I_3$$

$$I_s = V \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$

$$V = I_s \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)^{-1}$$

$$I_1 = I_s \frac{\frac{1}{R_1}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$


$$I_2 = I_s \frac{\frac{1}{R_2}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$

$$I_3 = I_s \frac{\frac{1}{R_3}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$

$$I_k = I_s \frac{\frac{1}{R_k}}{\sum_{j=1}^N \frac{1}{R_j}}$$
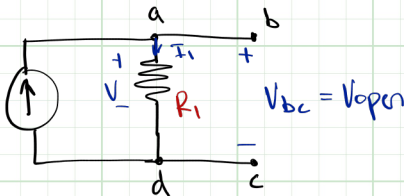
## Open Ckt Condition


- something with infinite resistance letting  $R_2 \rightarrow \infty$
- has voltage across it, but no current flows through



$$V_{bc} = V_{open} = V_{ad} = I_1 R_1 = I_s R_1 = V$$
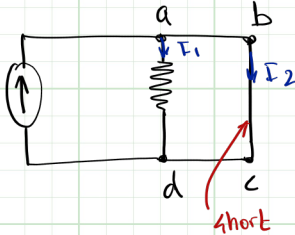
## Short Ckt Condition

- has zero resistance
- there is a current through a short, but no voltage across it.




$$I_1 = 0, I_2 = I_s$$

$$V_{ab} = V_{bc} = V_{\text{short}} = I_1 R_1 = 0$$
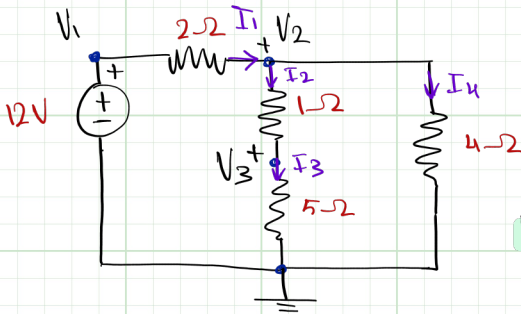
## Nodal Analysis

- Variable we solve is Voltage at nodes
- The law that you apply is KCL



Let  $N$  be # of nodes  
 $N_V$  be # of voltage sources

# of eqn needed


$$N - 1 - N_V = 4 - 1 - 1 = 2$$

$$V_1 = 12V$$


constrain

2 eqn. needed to solve ckt

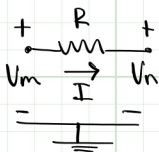- constrain condition is that  $V_1$  will always equal 12 V.




$$I = \frac{V_m - V_n}{R}$$

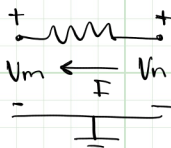

$$I = \frac{V_n - V_m}{R}$$



# Node Analysis Eg 1

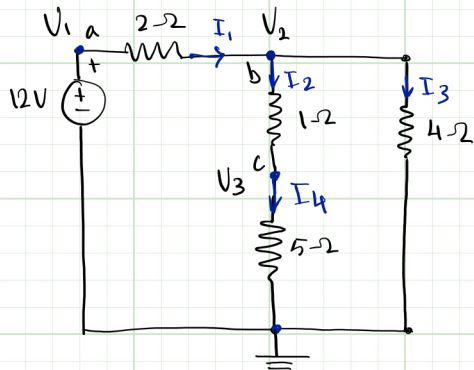

Find the node voltages and current through 5Ω resistor and power dissipated by it

$$I_2 = I_4$$

$$N-1-N_V = 4-1-1 = 2 \text{ eq.}$$

Constraint Condition :

$$V_1 = V_D \quad \rightarrow \quad V_1 = 12V$$

$$12 = V_1$$

b:  $I_1 = I_2 + I_3$

$$\frac{V_1 + V_2}{2} = \frac{V_2 - V_3}{1} + \frac{V_2 - 0}{4}$$

$$\frac{12 + V_2}{2} = V_2 - V_3 + \frac{V_2}{4} \quad (i)$$

$$\frac{1}{2}V_1 + \frac{1}{2}V_2 = V_2 - \frac{5}{6}V_2 + \frac{1}{4}V_2$$

$$\frac{1}{2}V_2 - V_2 + \frac{5}{6}V_2 - \frac{1}{4}V_2 = -\frac{1}{2}V_1$$

$$\frac{V_2}{12} = -\frac{1}{2}V_1 \Rightarrow V_2 = -6V_1 = -6(12) = \underline{\underline{-72V = V_2}}$$

c:  $I_2 = I_4$


$$V_2 - V_3 = \frac{V_3 - 0}{5}$$

$$V_3 = 5V_2 - 5V_3 \quad (ii)$$

$$6V_3 = 5V_2$$

$$V_3 = \frac{5}{6}V_2 = \underline{\underline{-60V = V_3}}$$

## Nodal Ckt 2

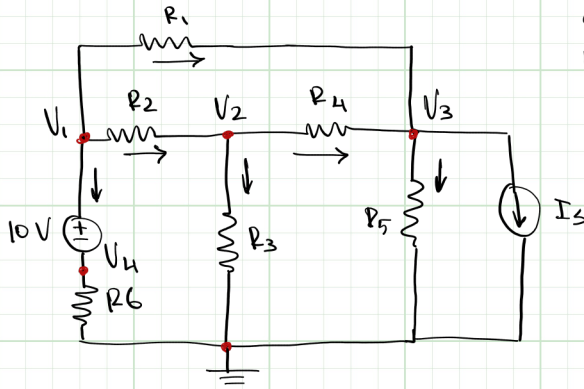

Write the equations that can be used to find the node voltages

$$N - 1 - N_V = 5 - 1 - 1 = 3$$

$$V_D = V_R$$

$$\underline{V_1 = V_4 + 10} \quad (\text{IV})$$

### Node 1

$$0 = \frac{V_1 - V_3}{R_1} + \frac{V_1 - V_2}{R_2} + \frac{V_4 - 0}{R_6} \quad (\text{I})$$


### Node 2

$$\frac{V_1 - V_2}{R_2} = \frac{V_2 - 0}{R_3} + \frac{V_2 - V_3}{R_4} \quad (\text{II})$$

### Node 3

$$\frac{V_1 - V_3}{R_1} + \frac{V_2 - V_3}{R_4} = \frac{V_3 - 0}{R_5} + I_s \quad (\text{III})$$

### Nodal Ckt 3

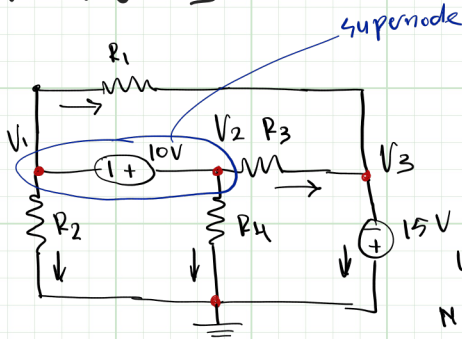

supernode

↳ 2 nodes that share same voltage source  
(none of the nodes are a reference node)

Write equations for node voltages

$$N - 1 - N_v = 4 - 1 - 2 = 1 \text{ eq.}$$

#### Constraint Conditions

$$V_1 = V_2$$

$$P_1 = P_2$$

$$V_3 + 15 = 0$$

$$V_1 + 10 = V_2$$


$$\underline{V_3 = -15}$$

$$\underline{V_2 = V_1 + 10}$$

#### Supernode

$$0 = \frac{V_1 - V_3}{R_1} + \frac{V_2 - V_3}{R_3} + \frac{V_2 - 0}{R_4} + \frac{V_1 - 0}{R_2}$$

### Modal Ckt 4

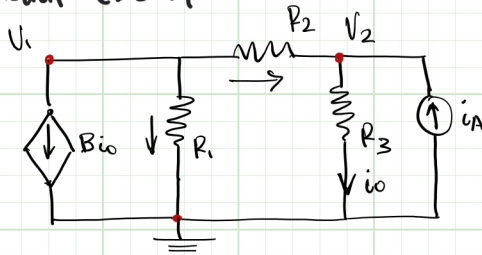

For dependent sources,  
express controlling variable  
( $i_o$ ) in terms of variables  
of interest (voltages)  
 $V_2 = i_o R_2 \Rightarrow i_o = \frac{V_2}{R_2}$

Assuming we know  $R_3$ ,  $i_A$ , and  $B$ , write down node voltages.

$N-1-MV = 3-1 = 2$  eq, no constraint cond.

Node 1

$$0 = B i_o + \frac{V_1 - V_2}{R_2} + \frac{V_1 + 0}{R_1}$$

$$0 = \frac{B V_2}{R_2} + \frac{V_1 - V_2}{R_2} + \frac{V_1}{R_1} \quad (I)$$


Node 2

$$\frac{V_1 - V_2}{R_2} + i_A = \frac{V_2 - 0}{R_3}$$

$$\frac{V_1 - V_2}{R_2} + i_A = \frac{V_2}{R_3} \quad (II)$$

# Nodal Eg

Find  $V_a, V_b, I_o$

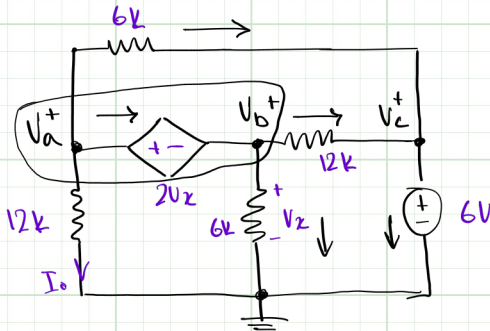

Supernode

$$CE = CL$$

$$0 = \frac{V_b - V_c}{12k} + \frac{V_b}{6k} + \frac{V_a - V_c}{6k} + \frac{V_a}{12k}$$

$$0 = \frac{V_b - 6}{12k} + \frac{V_b}{6k} + \frac{V_a - 6}{6k} + \frac{V_a}{12k}$$

$$0 = \frac{V_b - 6}{12k} + \frac{V_b}{6k} + \frac{3V_b - 6}{6k} + \frac{3V_b}{12k}$$

$$0 = \frac{V_b - 6 + 2V_b + 6V_b - 12 + 3V_b}{12k}$$

$$0 = \frac{12V_b - 18}{12k} \Rightarrow V_b = \frac{18}{12} = \frac{3}{2} V = V_b$$

$$N - 1 - N_v = 4 - 1 - 2 = 1$$

Constraints

$$V_b = V_x$$

$$V_c = 6V$$

$$V_a = 2V_x + V_b$$

$$V_a = 2V_b + V_b$$

$$V_a = 3V_b$$

$$V_a = 3\left(\frac{3}{2}\right) = \frac{9}{2} V$$

$$V_a = \frac{9}{2} V$$

$$I_o = \frac{V_a - 0}{12k} = \frac{9/2 V}{12k}$$

$$I_o = 3.75 \times 10^{-4} A$$

$$I_o = 0.375 mA$$

# Mesh Analysis

- Law used is KVL.
- Variable of interest is current in a loop/mesh.
- Number of equations:

$$\# \text{ indep. loops} - N_I = B - N + 1 - N_I$$

# of equations needed to solve mesh analysis ckt


# of branches

# of nodes

# of indep or dep current sources

$$V = IR$$

## Mesh Eg 1

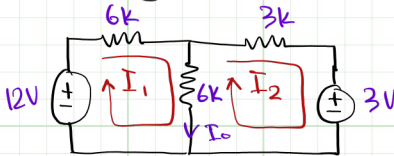

$$\begin{array}{cc} \text{Loop 1} & \text{Loop 2} \\ (I_1 - I_2) 6k & (I_2 - I_1) 6k \end{array}$$

for middle resistor

- plus at tail of arrow
  - resistors  $\rightarrow$  potential drop
- Find  $I_0$  in ckt.

For  $I_0$ , since it points in same direction as  $I_1$ ,  
 $I_0 = I_1 - I_2$

### Loop 1

$$PI = PD$$

$$12V = I_1 \cdot 6k + (I_1 - I_2) \cdot 6k \Rightarrow 12 = 6000 I_1 + 6000 (I_1 - I_2)$$

$$12 = 6000 I_1 + 6000 I_1 - 6000 I_2$$

$$12 = 12000 I_1 - 6000 I_2$$

$$+2(-3 = -6000 I_1 + 9000 I_2)$$

### Loop 2

$$PI = PD$$

$$0 = I_2 \cdot 3k + (I_2 - I_1) \cdot 6k + 3$$

$$-3 = 3000 I_2 + 6000 (I_2 - I_1)$$

$$-3 = 3000 I_2 + 6000 I_2 - 6000 I_1$$

$$-3 = 9000 I_2 - 6000 I_1$$

$$I_1 = (3 - 9000 (5 \times 10^{-4})) \div -6000 =$$


$$6 = 12000 I_2$$

$$I_2 = 5 \times 10^{-4} A$$



## Mesh Eg 2

Write loop eq. that solves circuit

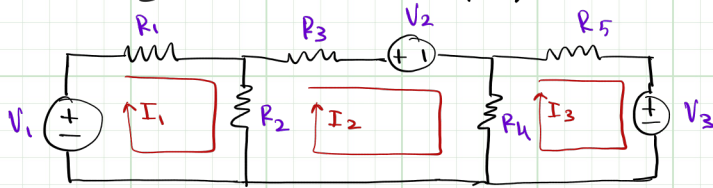

$$B - N + 1 - N_i = 8 - 6 + 1 - 0 = 3 \text{ eqn.}$$

Loop 1

$$PI = PD$$

$$V_1 = I_1 R_1 + (I_1 - I_2) R_2 \quad \checkmark$$

Loop 2

$$PI = PD$$


$$0 = I_2 R_3 + V_2 + (I_2 - I_3) R_4 + (I_2 - I_1) R_2 \quad \checkmark$$

Loop 3

$$PI = PD$$

$$0 = I_3 R_5 + V_3 + (I_3 - I_2) R_4 \quad \checkmark$$

# Mesh Eg 3

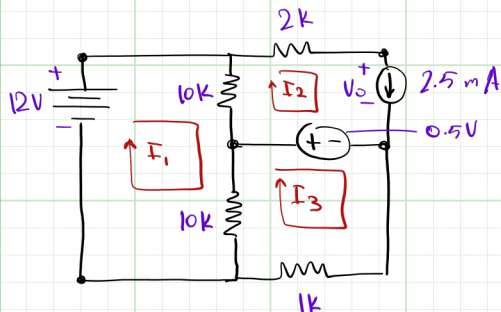

Find  $V_o$

$$B - N + 1 - N_i = 7 - 5 + 1 - 1 = 2 \text{ eq}$$

Constraint

$$I_2 = 2.5 \text{ mA}$$

because current source ensures this is always true

Loop 1

$$PI = PD$$

$$12V = (I_1 - I_2) \cdot 10k + (I_1 - I_3) \cdot 10k \quad (I) \quad \checkmark$$

Loop 2

$$PI = PD$$

$$0.5 = I_2 \cdot 2k + V_o + (I_2 - I_1) \cdot 10k \quad (II) \quad \checkmark$$

Loop 3

$$PI = PD$$

$$0 = 0.5 + I_3 \cdot 1k + (I_3 - I_1) \cdot 10k \quad (III) \quad \checkmark$$

~~$$(I) \quad 12 = 10000 I_1 - 10000 I_2 + 10000 I_1 - 10000 I_3$$~~

~~$$0 = 20000 I_1 - 10000 I_3 - 10000 (2.5 \times 10^{-3})$$~~

~~$$-25 = 20000 I_1 - 10000 I_3$$~~


~~$$(III) \quad 0 = 0.5 + 1000 I_3 + 10000 I_3 - 10000 I_1$$~~

~~$$-0.5 = -10000 I_1 + 11000 I_3$$~~

~~$$\begin{bmatrix} 20000 & -10000 & -25 \\ -10000 & 11000 & -0.5 \end{bmatrix} \sim \begin{bmatrix} 0 & 12000 & -26 \\ -10000 & 11000 & -0.5 \end{bmatrix}$$~~

~~$$\begin{bmatrix} 0 & 1 & -2.167 \times 10^{-3} \\ 1 & -1.1 & 5 \times 10^{-4} \end{bmatrix} \sim \begin{bmatrix} 0 & 1 & -2.167 \times 10^{-3} \\ 1 & 0 & -1.8837 \times 10^{-3} \end{bmatrix}$$~~

# Mesh Eg 4

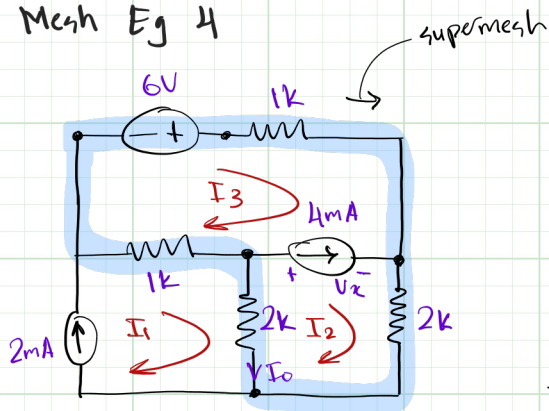

Find  $I_0$

2 meshes share  
a current source,  
you have a **supermesh**

## Constraints

$$I_1 = 2 \text{ mA} \quad \text{--- loop 1}$$

$$I_2 - I_3 = 4 \text{ mA} \quad \text{--- loop 3}$$

$$\hookrightarrow I_2 = I_3 + 4$$

$$= -\frac{2}{3} + 4 = \frac{10}{3} \text{ mA}$$

## KVL Supermesh

$$PI = PD$$

$$(6 \text{ V} = (I_2 \cdot 2 \text{ k}) + (I_2 - I_1) \cdot 2 \text{ k} + (I_3 - I_1) \cdot 1 \text{ k} + I_3 \cdot 1 \text{ k}) \div 1 \times 10^{-3}$$

$$6 \text{ mV} = 2I_2 + (I_2 - 2)2 + (I_3 - 2) + I_3$$

$$6 = 2(I_3 + 4) + (I_3 + 4 - 2)2 + I_3 - 2 + I_3 \quad (I \text{ in mA})$$

$$6 = 2I_3 + 8 + 2I_3 + 4 + I_3 - 2 + I_3$$


$$6 - 8 - 4 + 2 = 6I_3$$

$$I_3 = -\frac{2}{3} \text{ mA}$$

$$I_0 = I_1 - I_2$$

$$= 2 - \frac{10}{3} = -\frac{4}{3} \text{ mA}$$

$$\therefore I_0 = -\frac{4}{3} \text{ mA}$$

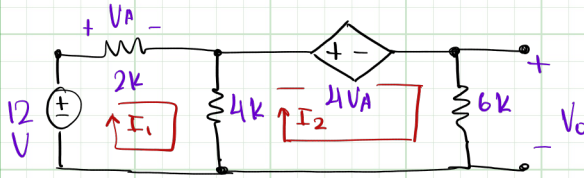Mesh Ckt With Dep. Source

$$B - N + 1 - N_i = 5 - 4 + 1 - 0 = 2 \text{ eq.}$$

Loop 1

$$PI = PD$$

$$\frac{12 \text{ V}}{1 \times 10^{-3}} = \frac{I_1 \times 2\text{k} + (I_1 - I_2) \times 4\text{k}}{1 \times 10^{-3}}$$

$$\begin{aligned} V &\rightarrow \text{mV} \\ I &\rightarrow \text{mA} \\ \text{k}\Omega &\rightarrow \Omega \end{aligned}$$

$$12 = 2I_1 + 4(I_1 - I_2)$$

$$\begin{aligned} 12 &= 2I_1 + 4I_1 - 4I_2 \\ 12 &= 6I_1 - 4I_2 \quad (\text{I}) \end{aligned}$$

Loop 2

$$PI = PD$$

$$0 = 4VA + 6I_2 + 4(I_2 - I_1)$$

$$0 = 8I_1 + 6I_2 + 4I_2 - 4I_1$$

$$0 = 4I_1 + 10I_2 \quad (\text{II})$$

$$V_0 = I_2 6$$

$$= -\frac{12}{19} \times 6 = -\frac{72}{19} \text{ V}$$

$$\begin{bmatrix} 6 & -4 & 12 \\ 4 & 10 & 0 \end{bmatrix} \sim \begin{bmatrix} 1 & -\frac{2}{3} & 2 \\ \frac{4}{10} & 1 & 0 \end{bmatrix} = \begin{bmatrix} 1 & -\frac{2}{3} & 2 \\ 0 & \frac{19}{15} & -\frac{4}{5} \end{bmatrix} \sim \begin{bmatrix} 1 & -\frac{2}{3} & 2 \\ 0 & 1 & -\frac{12}{19} \end{bmatrix}$$

$$\therefore V_0 = -3.8 \text{ [V]}$$

Find value of  $V_0$ 


Write the controlling variable in terms of variables of interest (mesh currents)

$$V_A = I_1 \times 2\text{k} = 2I_1$$

$$[\text{mV}], [\text{mA}], [\Omega]$$

## Mesh Ckt

Find  $V_o$

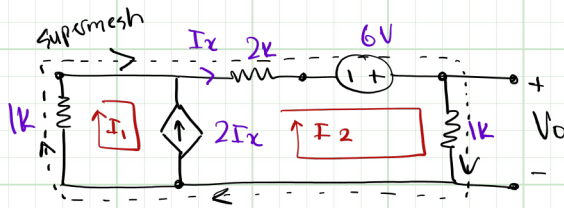

- supermesh
- dependent source

$$B - N + 1 - N_i = 5 - 4 + 1 - 1 = 1 \text{ eq.}$$

$$I_2 - I_1 = 2I_x = 2I_2 \Rightarrow I_2 - I_1 = 2I_2 \text{ (constraint)}$$

### Supermesh KVL

$$P.I = P.D$$

$$6\text{mV} = 2I_2 + I_2 + I_1$$

$$6 = 3I_2 - I_2 = 2I_2$$

$$I_2 = 3 \text{ mA}$$

$$I_1 = -I_2$$


$$= -3 \text{ mA}$$

$$V_o = I_2 \times 1\text{k}\Omega$$

$$= (3 \times 10^{-3}) \times 1 \times 10^3$$

$$V_o = 3 \text{ V}$$

## Mesh and Node Ckt

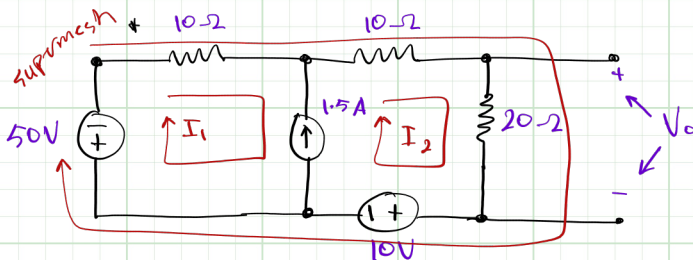

$$B - N + 1 - N_i = 6 - 5 + 1 - 1 = 1 \text{ eq.}$$

$$\text{constraint: } I_2 - I_1 = 1.5 \text{ A} \Rightarrow I_1 = I_2 - 1.5$$

### Supermesh KVL

$$P_I = P_D$$

$$0 = 10I_1 + 10I_2 + 20I_2 + 10 + 50$$

$$-60 = 10(I_2 - 1.5) + 30I_2$$

$$-60 = 40I_2 - 15$$


$$40I_2 = -45$$

$$I_2 = -\frac{9}{8}$$

$$V_o = 20I_2$$

$$= -\frac{9 \times 20}{8} = -22.5$$

$$\therefore V_o = -22.5 \text{ V}$$

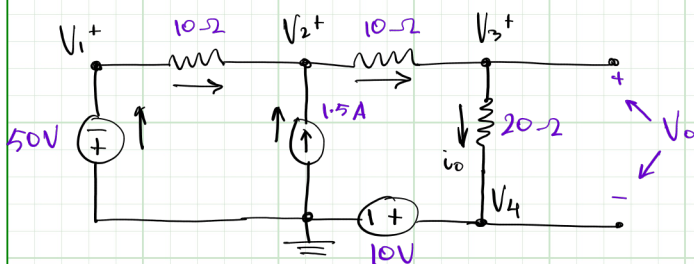

$$N - 1 - N_V = 5 - 1 - 2 = 2 \text{ eq}$$

$$\text{constraints: } V_1 = -50$$

$$V_4 = 10 \text{ V}$$

$$V_o = i_o R$$

### KCL at node 2

$$C_E = C_L$$

$$\frac{V_1 - V_2}{10} + 1.5 = \frac{V_2 - V_3}{10}$$

$$\frac{-50 - V_2}{10} + 1.5 = \frac{V_2 - V_3}{10}$$

### KCL @ node 3

$$\frac{V_2 - V_3}{10} = \frac{V_3 - V_4}{20}$$

$$\frac{V_2 - V_3}{10} = \frac{V_3 - 10}{20}$$

~~$$-50 - V_2 + 1.5 = \frac{V_2 - V_3}{10}$$~~

~~$$-35 = \frac{V_2 - V_3}{10}$$~~

~~$$V_2 = \frac{-35 + V_3}{10}$$~~

~~$$10V_2 - 10V_3 = V_3 - 10$$~~

~~$$10V_2 + 10 = 11V_3$$~~




~~$$V_2 = \frac{1}{10} \cdot \frac{-35 + V_3}{10} + 1$$~~

~~$$V_3 = \frac{10}{11} \cdot \frac{-35}{10} + \frac{10}{11} \cdot \frac{V_3}{10} + 10$$~~



~~$$V_3 - \frac{100}{121} V_3 = \frac{-350}{121} + 10$$~~

~~$$V_3 = \left( \frac{-350}{121} + 10 \right) \div \left( 1 - \frac{100}{121} \right) =$$~~

# Equivalence

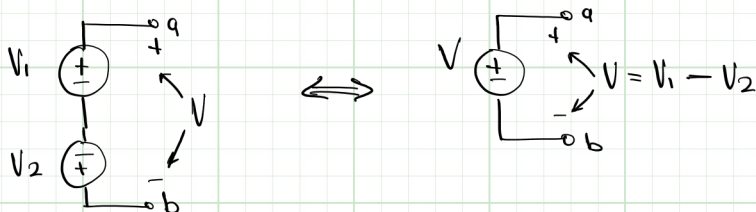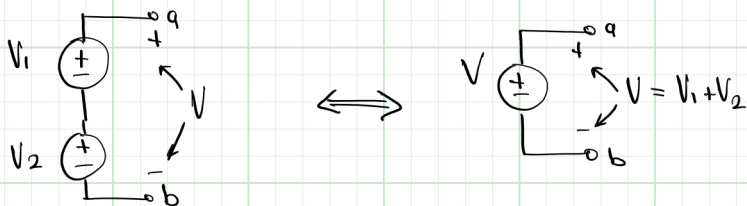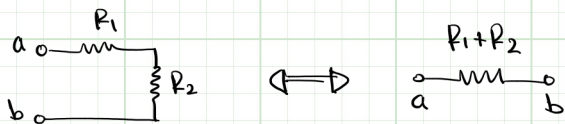

## Source Transform

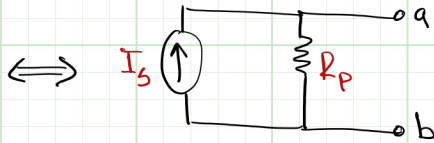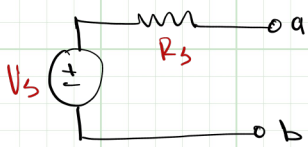

if

$$V_s = I_s R_s$$

$$R_s = R_p - R$$

- disable voltage by
- disable current by




# Source Transform Ex







Find pwr 6V battery

- repeatedly apply source transform to simplify ckt.
- switch between parallel + current src and series + voltage src

$$V_S = R_S I_S \quad | \quad R_P = R_S$$

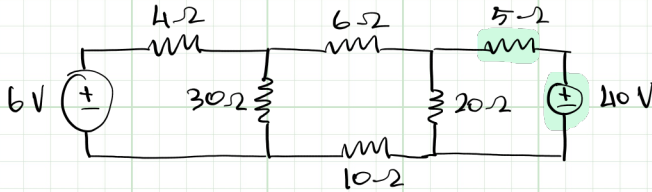

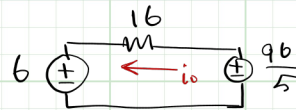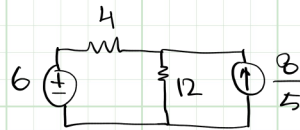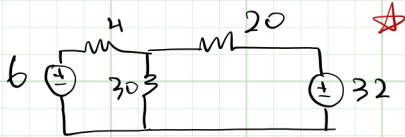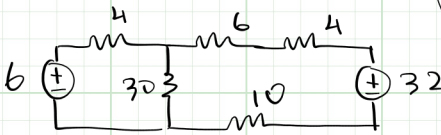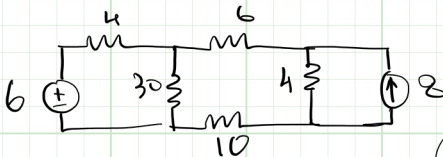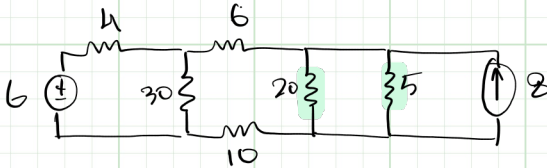Use source transform to find power in 12V battery.




$$i_o = \frac{\frac{96}{5} - 6}{16} = 0.825 \text{ A}$$

$$P = i_o \cdot V = (0.825)(6)$$

$$P = 4.95 \text{ W}$$

# Linearity

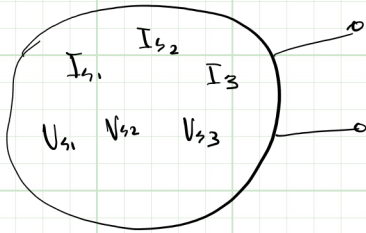

$$V_{out} = \alpha_1 V_{s1} + \alpha_2 V_{s2} + \alpha_3 V_{s3} + \dots$$

$$+ \beta_1 I_{s1} + \beta_2 I_{s2} + \beta_3 I_{s3}$$

→ Eg: We have ckt with indep.  $V_s$  and indep.  $I_s$ . We observe:

↳ when  $V_s = 10$  and  $I_s$  disabled,  $V_{out} = 3.5$

↳ when  $V_s = 10$  and  $I_s = 1$ ,  $V_{out} = 0.5$

Find  $V_o$  when  $V_s = 4$  [V] and  $I_s = 1$  [A]

$$3.5 = 10 V_s + 0 I_s$$

$$0.5 = 10 V_s + 1 I_s$$

$$\left. \begin{array}{l} 3.5 = 10 V_s + 0 I_s \\ 0.5 = 10 V_s + 1 I_s \end{array} \right\} V_{out} = \frac{7}{20} V_s - 3 I_s$$

$$\therefore V_{out} = -1.6V$$


$$V_{out} = \frac{7}{20} (4) - 3(1) = -1.6V$$

## Superposition

\* deactivate voltage source




\* deactivate current source

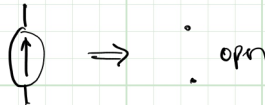

\* can use superposition for voltage and current, not power

\* careful when de-activating dependent source (better not to do it)

## Linearity and Scaling Eg

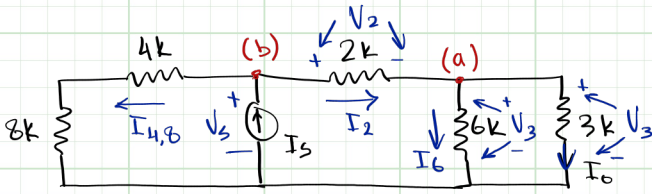

For this ckt, use linearity to calculate  $I_o$  when  $I_s = 6\text{ mA}$

1. Strategy: assume  $I_0$  is 1 mA and find  $I_5$ , then use linearity property to find  $I_0$  when  $I_5$  is 6 mA.

① If  $I_0 = 1\text{mA}$  and  $R = 3\text{k}$

$$V_3 = I_o R = (1 \text{ mA})(3 \text{ k}\Omega) = 3 \text{ V} = V_3$$

② If  $V_3 = 3V$  and  $R = 6k$

$$I_L = \frac{V_3}{R} = \frac{3V}{6k\Omega} = \frac{1}{2} \text{ mA} = I_L$$

③ Do KCL at node (a)

$$CE = CL$$

$$I_2 = I_6 + I_o = \frac{1}{2} \text{ mA} + 1 \text{ mA} = \frac{3}{2} \text{ mA} = I_2$$

④ If  $I_2 = \frac{3}{2} \text{ mA}$  and  $R = 2 \text{ k}\Omega$

$$V_2 = \left(\frac{3}{2} \text{ mA}\right) (2 \text{ k}\Omega) = 3 \text{ V}$$

⑤ Do KVL to find  $V_s$

$$V_S = V_2 + V_3 = 3 + 3 = 6 \text{ V} = V_S$$

⑥ Find  $I_{4,8}$  given  $V_s = 6V$  and combined  $R = 8+4 = 12k\Omega$

$$I_{4,8} = \frac{V_s}{R} = \frac{6V}{12k\Omega} = \frac{1}{2} mA$$

⑦ Find  $I_s$  by KCL @ b

$$I_3 = I_{4,8} + I_2 = \frac{1}{2} \text{ mA} + \frac{3}{2} \text{ mA} = \boxed{2 \text{ mA}}$$


Do Ratio

$$\frac{I_s}{I_o} = \frac{2}{1} = \frac{6}{I_{o\text{new}}}$$


$\therefore I_o = 3 \text{ mA}$
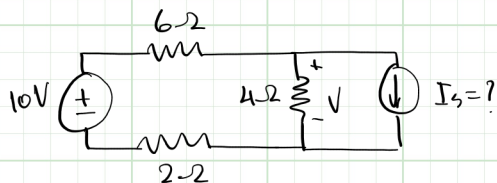
# Superposition Eg 1

What should be value of  $I_s$  if  $V$  (across  $4\Omega$  resistor) is zero. Use superposition




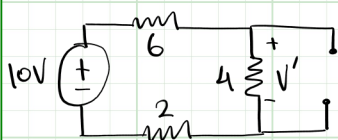→ First, disable the current source and find  $V'$



$$V' = 10 \cdot \frac{4}{6+2+4} = \frac{10}{3} [V]$$

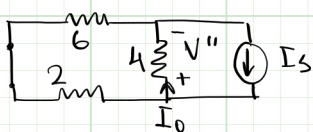→ Next, disable the voltage source and find  $V''$  and  $V'''$



$$4 \parallel (6 \leftrightarrow 2) \quad 4 \parallel 8 \quad - \downarrow V'' \equiv \downarrow V'''$$

$$I_0 = I_s \cdot \frac{\frac{1}{4}}{\frac{1}{4} + \frac{1}{8}} = \frac{2}{3} I_s [A]$$



$$V'' = 4 I_0 = \frac{8}{3} I_s [V]$$

$$V''' = -V'' = -\frac{8}{3} I_s [V]$$



$$V = V' + V''' = \frac{10}{3} - \frac{8}{3} I_s = 0$$

$$\frac{10}{3} = \frac{8}{3} I_s \Rightarrow I_s = \frac{10}{8} = \frac{5}{4} [A] = I_s$$

## Superposition Eg 2

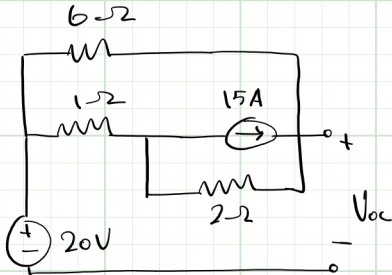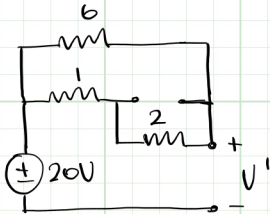Use superposition to find  $V_{oc}$ → First disable  $I_s$  (get  $V'$ )→ Second disable  $V_s$  (get  $V''$ )→  $V_{oc} = V' + V''$ 

$$V' = 20 \text{ [V]}$$

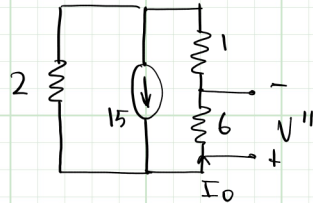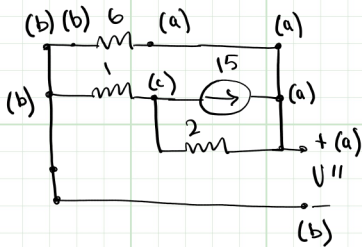

$$2 \parallel (1 \leftrightarrow 6)$$

$$2 \parallel 7$$

$$I_0 = 15 \cdot \frac{\frac{1}{7}}{\frac{1}{7} + \frac{1}{2}} = \frac{10}{3} \text{ [A]}$$

$$V_{oc} = V' + V'' = 20 + 20 = 40 \text{ [V]}$$


$$V' = 6 I_0 = 20 \text{ [V]}$$

$$\therefore V_{oc} = 40 \text{ [V]}$$




# Superposition Eg 3

Use superposition to find  $I_o$

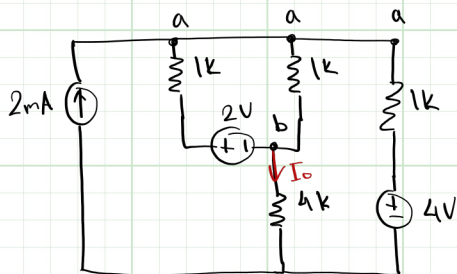

- Find  $I_o'$  with 2V alone
- Find  $I_o''$  with 4V alone
- Find  $I_o'''$  with 2mA alone

1k

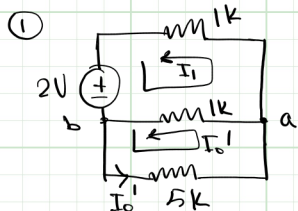

$$1k \parallel 1k \parallel (4k \leftrightarrow 1k)$$

$$1k \parallel 1k \parallel 5k$$

$$0 = (I_1 - I_o')1k + 1kI_1 + 2$$

$$0 = 1kI_1 - 1kI_o' + 1kI_1 + 2$$

$$-2 = -1kI_o' + 2kI_1 \quad (\text{eq. 1})$$

$$0 = 5kI_o' + (I_o' - I_1)1k$$


$$0 = 5kI_o' + 1kI_o' - 1kI_1$$

$$0 = 6kI_o' - 1kI_1 \quad (\text{eq. 2})$$

$$I_1 = -1/5500$$

$$I_o' = -3/2750$$

# Thevenin and Norton Equivalent Ckt

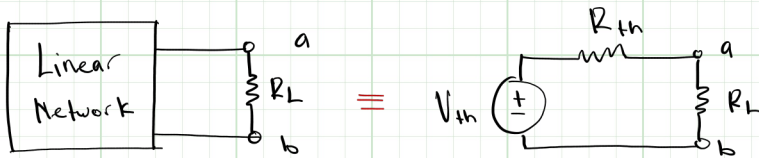

↓ source transform

$$V_{th} = I_N R_{th}$$

$$\text{and } R_{th} = R_N$$




### How to find $V_{th}$

- Go to terminal of interest, open it, and measure the open ckt voltage


### How to find $R_{th}$

- Go to terminal of interest, short it, calculate short ckt current, and find  $R_{th} = \frac{V_{th}}{i_{short}}$

### Thevenin Eg 1

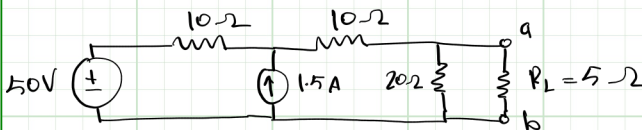

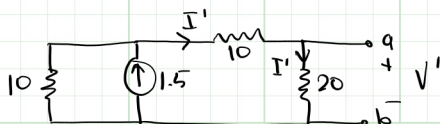Find  $V_{th}$  wrt terminals a-b where  $R_L = 5\Omega$  and also  $R_{th}$



$$I' = 1.5 \cdot \frac{1}{\frac{1}{10} + \frac{1}{30}} = \frac{3}{8} \text{ [A]}$$


$$V' = 20I' = \frac{15}{2} \text{ [V]}$$



$$V'' = 50 \cdot \frac{20}{10+10+20} = 25 \text{ [V]}$$

$$\therefore V_{oc} = V' + V'' = \frac{15}{2} + 25 = \frac{65}{2} = 32.5 \text{ [V]}$$
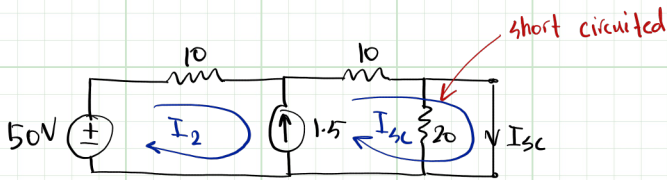
$$\therefore V_{oc} = V_{Th} = 32.5 \text{ [V]}$$



Supermesh KVL  $1.5 = I_{sc} - I_2 \quad (eq.1)$

$$50 = 10I_2 + 10I_{sc} \quad (eq.2)$$

$$I_{sc} = \frac{13}{4} \text{ [A]}$$


$$I_2 = \frac{7}{4}$$

$$R_{Th} = \frac{V_{Th}}{I_{sc}} = \frac{32.5}{3.25} = 10 \Omega$$


$$\therefore R_{Th} = 10 \Omega$$


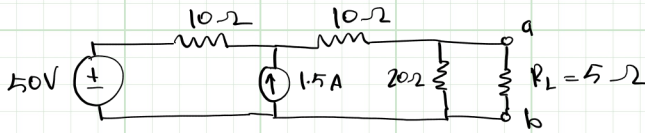
# Thevenin Eg 1 *see last lecture note for full solution*




change into

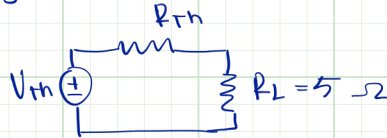


## Formula

- if only have independent sources
- shortcircuit with  $R_{th}$ 
  - ↳ 1) deactivate all sources (voltage and current)
  - 2) look back and ask "what is equivalent resistance of remaining things)
  - 3)  $R_{eq} = R_{th}$

## Note

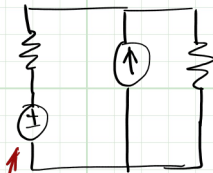


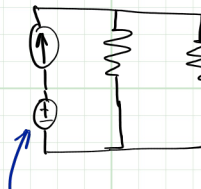
*not a current divider  
because Voltage  
s/c is on diff branch*



*Yes, current divider  
because  $V_s$  on same  
branch as  $I_s$*
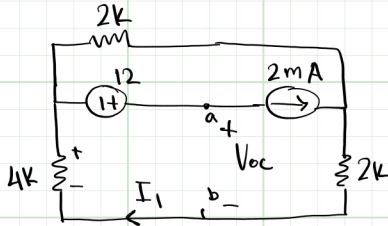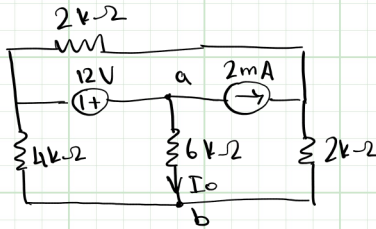
## Thevenin Eg: 2

Use the Thevenin equivalent ckt to find the  $I_o$





$$I_1 = 2(10^{-3}) \cdot \frac{\frac{1}{6 \times 10^3}}{\frac{1}{2 \times 10^3} + \frac{1}{6 \times 10^3}} = 5 \times 10^{-4} \text{ [A]}$$

KVL:  $P_I = P_D$

$$V_{oc} = 12 + 4k(-5 \times 10^{-4}) = 10 \text{ [V]}$$


$$\therefore V_{Th} = 10 \text{ [V]}$$

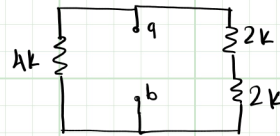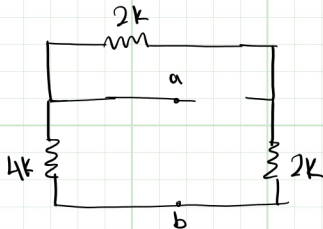

$$4k \parallel (2k \leftrightarrow 2k) = \left( \frac{1}{4k} + \frac{1}{2k+2k} \right)^{-1}$$

$$\therefore R_{eq} = R_{Th} = 2000 \Omega$$

$$\therefore R_{Th} = 2k\Omega$$

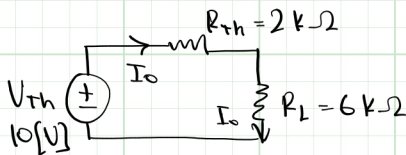


$$V_L = 10 \cdot \frac{6k}{2k+6k} = \frac{15}{2} \text{ [V]}$$


$$I_o = \frac{V_L}{R_L} = \frac{15/2}{6k} = 1.25 \times 10^{-3} \text{ [A]}$$

$$\therefore I_o = 1.25 \text{ mA}$$


### Thevenin Eg 3

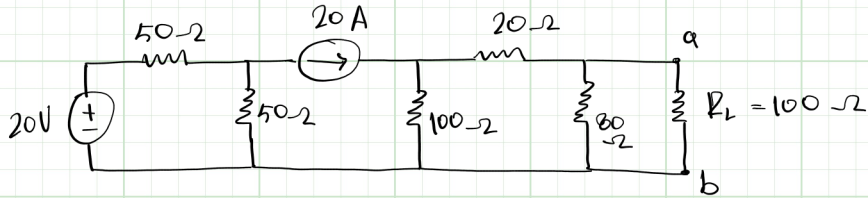

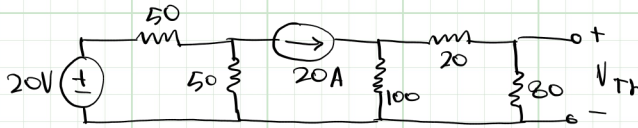Find the Thevenin Equivalent Ckt for the ckt at terminal a-b and find power dissipated by  $R_L$ .



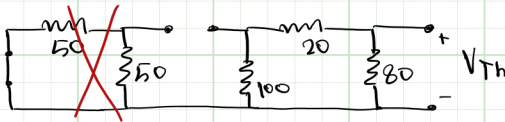
$$V_{Th} = 10[A] \times 80[\Omega] = \underline{800[V]} = V_{Th}$$



$$R_{Th} = R_{eq} : (100 \leftrightarrow 20) \parallel 80$$

$$\left( \frac{1}{120} + \frac{1}{80} \right)^{-1} = 48[\Omega]$$
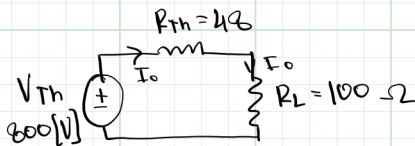
$$\therefore R_{Th} = \underline{48[\Omega]}$$



$$V_{Th} = I_o R_{eq}$$


$$I_o = \frac{800}{48 + 100} = \frac{200}{37}$$

$$P = I_o^2 R = \left( \frac{200}{37} \right)^2 (100)$$

$$\therefore P = 2921.84[W]$$
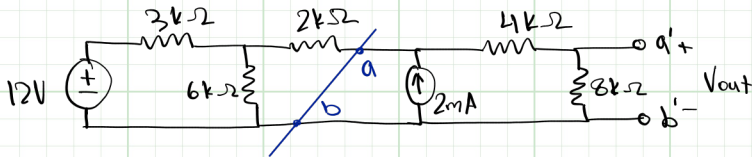
## Thvenin Breaking Ckt


- when breaking a ckt with dependent source, make sure you keep dependent src and its controlling parameter on same side.




Use Thevenin twice to find  $V_{out}$  (break the ckt at a-b)




# Thevenin Ckts : Dependent Sources

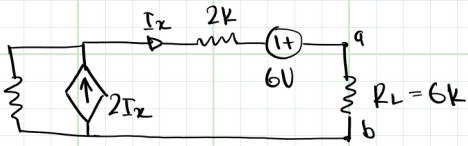

## Thevenin Ckt Dependent

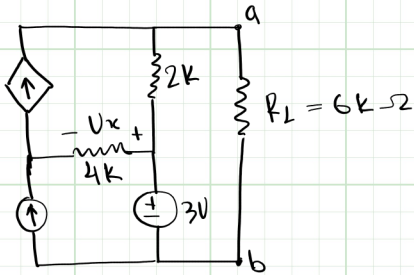


Thevenin Eg 3  $V_{th}$  is zero

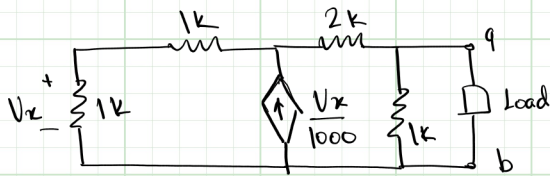

- when you have no dependent src,  $V_{th} = 0$ .
- To find  $R_{th}$ , attach battery and
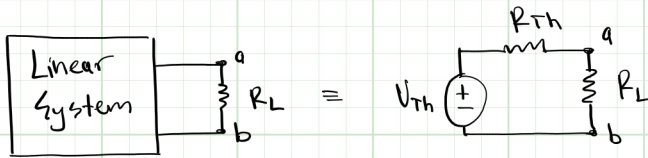
## Maximum Power Transfer

• If load has  $R_{Th}$ , then maximum power is transferred



For max power transfer, set  $R_L = R_{Th}$

$$\text{Max Power} = \frac{(V_{Th})^2}{4R_{Th}} = \frac{(V_{Th})^2}{4R_L}$$



## Week 9: Lec 2

- When calculating  $R_{Th}$ , it must be (+).


↳ Let's you check if  $V_{Th}$  and  $I_{sc}$  are correct

- If ckt has dependent sres, break it and find Thevenin ckt

↳ when you attatch it back, your new ckt has no more dependent ckt → you can easily find  $R_{Th}/R_L$ .

- For good Thevenin breaking ckt **check Lec 29 Examples**

## Transient for 1st Order CKT

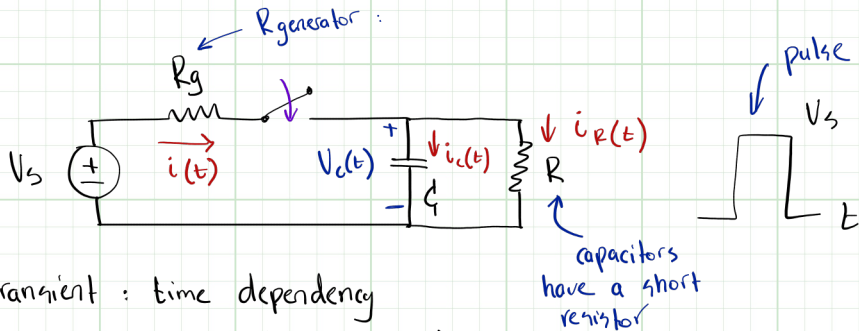

- transient: time dependency
- source is still a battery (DC)
- 1st Order because 1 storage element (one type, like inductor or capacitor)  
 ↳ if 2 of them same kind → can combine



- doesn't happen instantaneously
- takes

- Every battery: resistor
- Every capacitor:
- Every inductor:

→ At  $t = t_0$  → we close switch

what is  $V_c(t)$ ?

not  
function  
of time

$$i(t) = i_c + i_R$$

$$\frac{V_s - V_c}{R_g} = C \frac{dV_c(t)}{dt} + \frac{V_c(t)}{R}$$

differential  
equation

$$C \frac{R_g R}{R_g + R} \frac{dV_c(t)}{dt} + V_c(t) = V_s \cdot \frac{R}{R + R_g}$$

- 1st order linear nonhomogeneous ODE

General Form

$$\tau \left[ \frac{dx(t)}{dt} + x(t) = x(\infty) \right]$$

time constant  $\leftarrow$  controls how fast steady state is reached  
 $\tau = (R_g || R)$

$x(\infty) = x(t \rightarrow \infty)$   
 steady state

Solution Method

$\rightarrow$  Guess  $x(t) = k_1 + k_2 e^{-t/\tau}$

$\rightarrow \tau \left( -\frac{1}{\tau} \right) k_2 e^{-t/\tau} + k_1 + k_2 e^{-t/\tau} = x(\infty)$

$-k_2 e^{-t/\tau} + k_1 + k_2 e^{-t/\tau} = x(\infty)$

$\therefore \underline{x(\infty) = k_1}$

$\rightarrow$  given  $x(t_0) = x(t=0) = x(0)$

$x(0) = k_1 + k_2 e^{-0/\tau}$

$x(0) = k_1 + k_2$

$x(0) = x(\infty) + k_2$

$\therefore \underline{k_2 = x(0) - x(\infty)}$

$0^+$ : tiny instant after switch close

Full solution :

$$x(t) = \underbrace{x(\infty)}_{k_1} + \underbrace{[x(0^+) - x(\infty)]}_{k_2} e^{-\frac{t}{\tau}}$$

At different time instead of  $t=0$

$$x(t_0^+) = k_1 + k_2 e^{-t/\tau}$$

$$\Rightarrow k_2 = \left[ x(t_0^+) - x(\infty) \right] e^{t_0/\tau}$$

Full solution: 
$$x(t) = x(\infty) + \left[ x(t_0^+) - x(\infty) \right] e^{-(t-t_0)/\tau}$$

delayed time


$$\therefore V_c(t) = V_s \frac{R}{R+R_g} + \left[ 0 - \frac{R}{R+R_g} \right] e^{-\frac{t}{\tau}}$$

$$\tau = C \cdot \frac{R_g R}{R_g + R} = C (R \parallel R_g) \quad R \parallel R_g$$

as  $t \rightarrow \infty$ , the  $e^{-\frac{t}{\tau}}$  term goes to zero



$$\therefore V_c(t) = V_s \cdot \frac{R}{R+R_g}$$

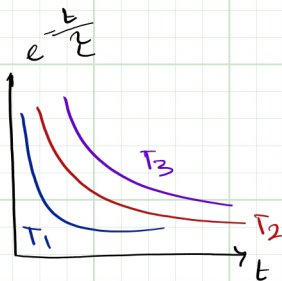meaning it makes sense because the  $C$  is like an open ckt --- voltage divider equ. matches




$$\tau_1 > \tau_2 > \tau_3$$

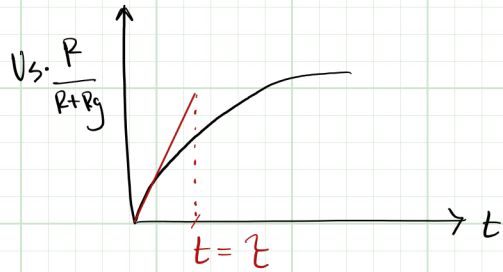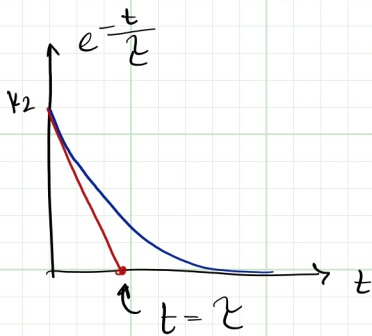+ larger the  $\tau$ , quicker the charging



Now, We Open Switch at  $t = t_0$

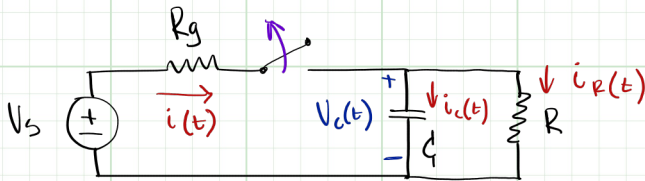

$$i_c(t) + i_R(t) = 0$$

$$C \frac{dV_c(t)}{dt} + \frac{V_c(t)}{R} = 0$$

$\Rightarrow$  canonical form

$$\boxed{CR \frac{dV_c(t)}{dt} + V_c(t) = 0}$$

steady state

$$\therefore V(\infty) = 0$$

$$\tau = RC$$

$$V_c(t_0^+) = V_s \frac{R}{R+R_g}$$

initial condition

$$\therefore V_c(t_0^+) = V_c(t_0^-)$$

discharging

$$V_c(t) = 0 + \left[ V_s \frac{R}{R+R_g} - 0 \right] e^{-t/RC}$$



$$V_c(t) =$$



Notes

- The voltage across capacitors must be continuous


$$i_c = C \frac{dV_c(t)}{dt}$$

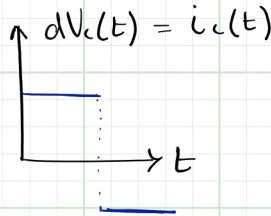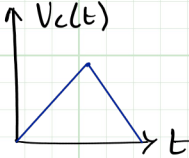

- The current through inductors must be continuous

Step-by-step Method

$$i_c = C \frac{dV}{dt}$$

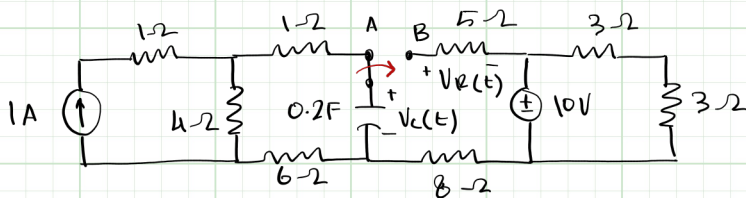


$$x(t) = x(\infty) + [x(0^+) - x(\infty)] e^{-\frac{t}{\tau}} \leftarrow$$

$$V_c(t) = V_c(\infty) + [V_c(0^+) - V_c(\infty)] e^{-\frac{t}{\tau}}$$

$$V_R(t) = V_R(\infty) + [V_R(0^+) - V_R(\infty)] e^{-\frac{t}{\tau}}$$

Find  $V_c(0^-)$ 

$$-\infty < t < 0^-$$

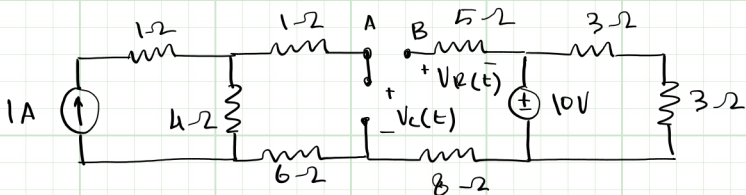

$$\Rightarrow V_c(0^+) = V_c(0^-) = (1 \text{ [A]}) (4 \text{ [}\Omega\text{]}) = 4 \text{ V} = V_c(0^+)$$


Find  $V_R(0^-)$ 

$\Rightarrow$  for resistor,  $V_R(0^+) \neq V_R(0^-)$  bc.  $V_R = i_R R$   $\leftarrow$  can be discontinuous

$$V_R(0^-) = (0 \text{ [A]}) (5 \text{ [}\Omega\text{]}) = 0 \text{ V} = V_R(0^-)$$

Finding  $V_R(0^+)$ : During switching, we can replace capacitor with a voltage src of voltage  $V_c(0^+) = V_c(0^-)$

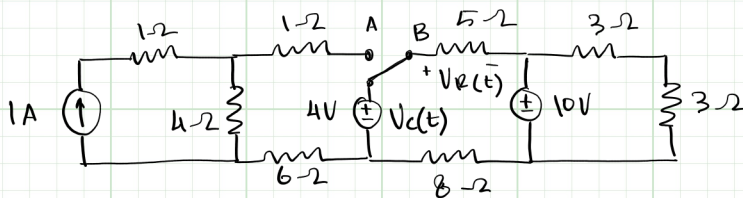
• Note: for inductors, replace with current src.



Do any method to find  $V_R$

↳ find  $V_R(0^-) = -2.3 \text{ [V]}$

Find  $V_C(\infty)$  and  $V_R(\infty)$

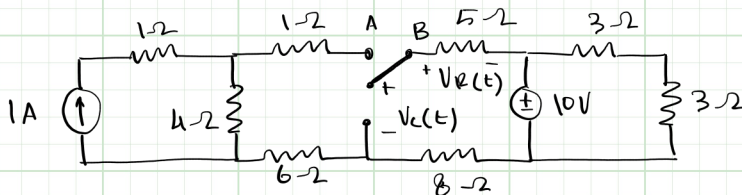

$$\therefore V_C(\infty) = 10 \text{ V}$$

$$V_R(\infty) = 0 \text{ V}$$

Findings

For capacitor:  $V_C(0^+) = V_C(0^-) = 4 \text{ V}$


$$V_C(\infty) = 10 \text{ V}$$

For



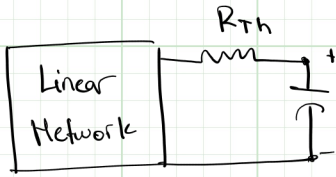
## Find Time Constant

terminal is where the capacitor was after switch is flipped




capacitive ckt:  $\tau = C R_{Th}$

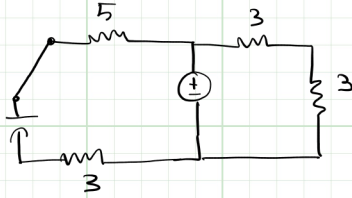


## Inductor Ckt

$$V_L = L \frac{di_L(t)}{dt}$$

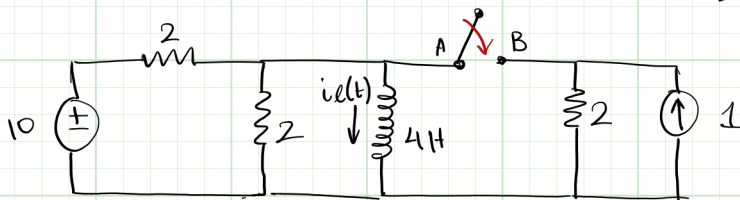

$$i_L(t) = i_L(\infty) + [i_L(0^+) - i_L(\infty)] e^{-\frac{t}{\tau}}$$
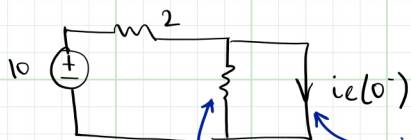
$$\rightarrow i_L(0^-) = i_L(0^+) = 5 \text{ [A]}$$




$$i_L(0^-) = \frac{10}{2} = 5 \text{ [A]}$$

inductor is a short to DC  
gets shorted

## Find $i_L(\infty)$

\* looks like short


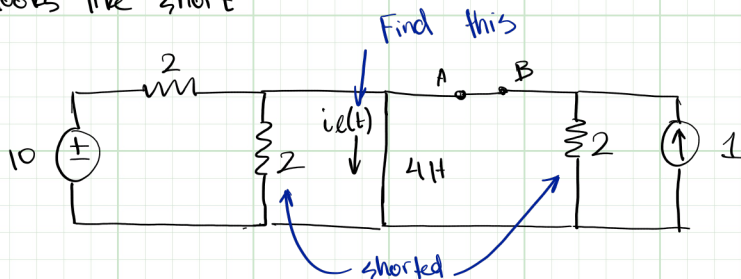


Use nodal:  $\rightarrow$  get  $i_L(\infty) = 6 \text{ [A]}$

\* For inductors:  $\tau = \frac{L}{R_{th}}$

$$\therefore i_L(t) = 6 + [5 - 6] e^{-t/6} = 6 - e^{-t/6}$$

## Inductor Eg

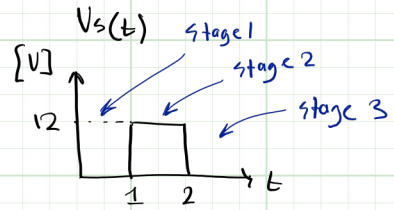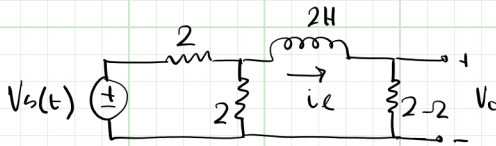

Find  $V_o(t)$  for  $-\infty < t < 1$   
 $1 < t < 2$   
 $2 < t < \infty$

stage 0:  $V_o(t) = 0 [V] \quad t \in (-\infty, 1)$

stage 1:  $V_o(t) = V_o(\infty) + [V_o(t=1^+) - V_o(\infty)] e^{-t/\tau}$

$\swarrow$  stage 1       $\nearrow$  stage 1       $\nearrow$  stage 1

$\Rightarrow$  We know  $V_o(t=1^-) = 0 [V]$ , but  $V_o = i_L R$ , so the voltage across resistor doesn't have to be cont.

$\Rightarrow$  However, I see that  $V_o$ 's resistor is fed by  $i_L$ , and since  $i_L$  has to be continuous  $\rightarrow \therefore V_o$  is continuous

$$\therefore V_o(t=1^-) = V_o(t=1^+) = 0 [V]$$

$\Rightarrow$  To find  $V_o(\infty)$ , replace inductor with a short and find  $V_o$  in that case  $\rightarrow V_o(\infty) = 4 [V]$

$$\Rightarrow \tau = \frac{L}{R_{th}} = \frac{3}{2}$$

as seen by inductor after event has happened

$$V_o(t) = 4 \left[ 1 - e^{-\frac{(t-1)}{3/2}} \right], \quad t \in (1, 2)$$

Stage 2:  $V_o(t) = V_o(\infty) + [V_o(t=2^+) - V_o(\infty)] e^{-t/\tau}$

stage 2

⇒ Notice that  $R_{in}$  in stage 2 hasn't changed from stage 1

∴  $\tau$  is the same →  $\tau = \frac{3}{2} \text{ s}$

⇒ as  $t \rightarrow \infty$ ,  $V_o(\infty) \rightarrow 0$  because  $V_s(t)$  is zero

∴  $V_o(\infty) = 0 \text{ [V]}$

⇒ Finding  $V_o(t=2^+) = V_o(t=2^-)$  because voltage across resistor is fed by  $i_e$ , which is always continuous

⇒ so we plug in to eq. 2

$$V_o(t=2^-) = 4 \left[ 1 - e^{-\frac{(2-1)}{3/2}} \right] = 3.11 \text{ [V]} = V_o(t=2^+)$$

$$\therefore V_o(t) = 0 + 3.11 e^{-\frac{(t-2)}{3/2}} \text{ [V]}, \quad t \in (2, \infty)$$

# Sinusoidal Excitation (AC-Intro)

- needs complex algebra



$$x(t) = A \cos(\omega t + \phi)$$

peak amplitude  
(distance from  
x-axis to peak)

angular  
frequency  
 $\left[\frac{\text{rad}}{\text{s}}\right]$


phase angle  
[rad] or [degree]

- peak-to-peak amplitude: double of peak amplitude

- period ( $T$ ) of a function:  $T = \frac{2\pi}{\omega}$

- regular frequency  $2\pi f = \omega$  or  $f = \frac{1}{T}$  [Hz]

## Leading & Lagging

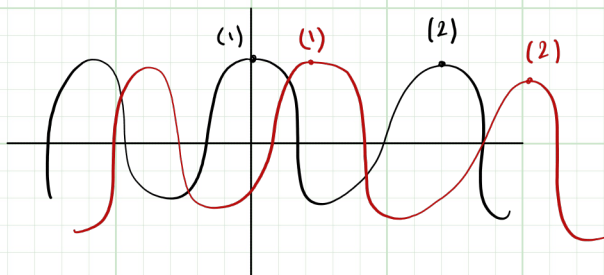

- 1) must have same frequency
- 2) all must be in  $\sin$  or all in  $\cos$ 
  - $\hookrightarrow \sin(\omega t + \phi) = \cos(\omega t + \phi - \pi/2)$
  - $\hookrightarrow \cos(\omega t + \phi) = \sin(\omega t + \phi + \pi/2)$
- 3) peak amplitude must be all same sign
  - $\hookrightarrow -\sin(\omega t + \phi) = \sin(\omega t + \phi - \pi)$
  - $\hookrightarrow -\cos(\omega t + \phi) = \cos(\omega t + \phi + \pi)$
- 4) difference must be less than  $180^\circ$  or  $\pi$  rad
  - $\hookrightarrow$  we can add  $360^\circ$  to argument and nothing changes

Eg: 2

## Complex Numbers $j = \sqrt{-1}$ or $j^2 = -1$

• complex number:  $\boxed{z = x + jy}$ ,  $z \in \mathbb{C}$ ,  $x, y \in \mathbb{R}$

$x = \operatorname{Re}(z)$   $y = \operatorname{Im}(z)$

• complex conjugate:  $\boxed{z^* = x - jy}$

• identity:  $\boxed{z \cdot z^* = x^2 + y^2 \in \mathbb{R}}$

## Complex Exponential and Polar Form

Euler Identity:  $\boxed{Ae^{j\alpha} = A\cos\alpha + jA\sin\alpha}$

$z = x + jy = Ae^{j\alpha} = A\cos\alpha + jA\sin\alpha$  complex exponential

•  $x = A\cos\alpha$

•  $A = \sqrt{x^2 + y^2}$

•  $y = A\sin\alpha$

•  $\alpha = \arctan\left(\frac{y}{x}\right)$

• polar representation:  $\boxed{Ae^{j\alpha} = A \angle \alpha}$

## Phasors

AC:  $V(t) = V_m \cos(\omega t + \alpha_v)$

or  $V(t) = V_m \sin(\omega t + \alpha_v)$

- We will convert from ODE to algebraic equations, but we have to use complex numbers

Let  $V(t) = V_m \cos(\omega t + \alpha_v)$

$$V(t) = \operatorname{Re} [V_m e^{j(\omega t + \alpha_v)}] = \operatorname{Re} [V_m e^{j\alpha_v} e^{j\omega t}]$$

doesn't depend on t

$$= \operatorname{Re} [\underline{V} e^{j\omega t}]$$

where  $\boxed{V_m e^{j\alpha_v} = \underline{V}}$  is called a **phasor**

- phasor is the part that does not depend on time

Proof:

$$\operatorname{Re} [V_m \cos(\omega t + \alpha_v) + j \sin(\omega t + \alpha_v)] = V_m \cos(\omega t + \alpha_v)$$

real part, no j

- if given  $V(t)$  or  $i(t)$  as a sin, convert to cos function and then take real part of it.

Eg: given  $i(t) = I_m \sin(\omega t + \alpha_i)$

$$i(t) = I_m \cos(\omega t + \alpha_i - \frac{\pi}{2}) = \operatorname{Re} [I_m e^{j(\omega t + \alpha_i - \frac{\pi}{2})}]$$

$$\underline{I} = I_m e^{j(\alpha_i - \frac{\pi}{2})} = \operatorname{Re} [I_m \cdot e^{j\omega t} \cdot e^{j(\alpha_i - \frac{\pi}{2})}]$$

so phasor is



## Phasor Relationship for RLC

- phasor representation / domain
- frequency domain
- sinusoidal steady state

Resistor:  $V_R(t) = i(t)R \Rightarrow \underline{V} = R \underline{I}$   $V_{me} = R I_{me}$

Inductor:  $V_L(t) = L \frac{di(t)}{dt} \Rightarrow \underline{V_L} = j\omega L \underline{I}$

Capacitor:  $i_C(t) = C \frac{dV_C(t)}{dt} \Rightarrow \underline{V_C} = \frac{1}{j\omega C} \underline{I_C}$

time domain                      phasor domain

$V_{me} = R I_{me}$

impedances

- if the real part of 2 phasors are equal, then the 2 phasors are equal.

Register  $\xrightarrow{R}$   $\xrightarrow{R}$

→ For  $V_m e^{j\omega t} = R I_m e^{j\omega t}$  to be true, we know that  $V_m = R I_m$  and  $\omega V = \omega R I$

→ For resistors, the voltage and current are in phase

Inductor  $\xrightarrow{\quad}$   $j\omega L$

→ For  $V_m e^{j\omega t} = j\omega L I_m e^{j\omega t}$ , impedance is  $j\omega L$   
 ↳ unit of  $[-2]$ , so

$$V_m \angle \phi_v = j\omega L I_m \angle \phi_i$$

Since  $j = e^{j\frac{\pi}{2}} = 1 \angle \frac{\pi}{2} = 1 \angle 90^\circ$

$$V_m \angle \phi_v = \omega L I_m \angle \phi_i + 90^\circ$$

$$\theta_i = \theta_v - 90^\circ$$


→ For inductors, Voltage leads current by  $90^\circ$ .

Capacitor  $\xrightarrow{\zeta} \Rightarrow \rightarrow \frac{1}{j\omega\zeta} = \frac{-j}{\omega\zeta}$

$$U_m e^{j\omega t} = I_m e^{j\omega t} \frac{1}{j\omega L}$$

$$\theta_v = \theta_i - 90^\circ$$

→ For capacitors, current leads voltage by  $90^\circ$ .

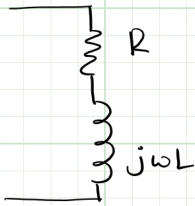AC Eg 1

$$Z = 5 + j4$$

$$Z = 5$$

$$j\omega_1 L = j4$$

$$\omega_1 L = 4$$

$$L = \frac{4}{\omega_1}$$

$$\omega_1 = 1000 \text{ rad/s}$$


$$\omega_2 = 1300 \text{ rad/s}$$

$$j\omega_2 L = j\omega_2 \left( \frac{4}{\omega_1} \right)$$

$$= j \left( \frac{1300}{1000} \right) 4$$

$$= \boxed{j4.4}$$

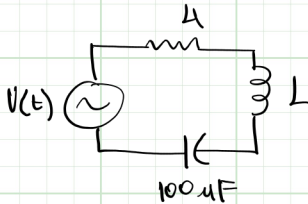- \* to make things in same phase,  
make sure arctan portion is 0.



$$A_m \cos(\omega t + \phi) \rightarrow A_m \angle \phi$$

$$A_m \sin(\omega t + \phi) \rightarrow A_m \cos(\omega t + \phi - \frac{\pi}{2}) \rightarrow A_m \angle \phi - \frac{\pi}{2}$$

Impedance:  $Z = R + jX$

impedance  $\swarrow$   $\nwarrow$  resistance  $\swarrow$  reactance

$G$  is not  $\frac{1}{R}$

Admittance:  $Y = \frac{1}{Z} = G + jB$

$\swarrow$  admittance  $\nwarrow$  conductance  $\swarrow$  susceptance

$$G = \frac{R}{R^2 + X^2}$$


$$B = \frac{-X}{R^2 + X^2}$$

$$R = \frac{G}{G^2 + B^2}$$

$$X = \frac{-B}{G^2 + B^2}$$

$\rightarrow$  admittance combine in opposite way to  $\parallel$  and  $\leftrightarrow$  impedances

AC Eg

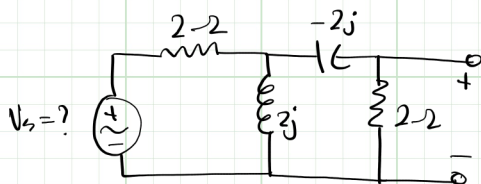


$$V_o = 8 \angle 45^\circ$$

- \* To solve ckt with both DC and AC sources  
 $\rightarrow$  use superposition by disabling each source and adding them up algebraically.
- \* Once you find sum of AC part (in phasor domain)  
 $\rightarrow$  multiply by  $e^{j\omega t}$  and take real part (should get cos function)
- \* At resonance frequency  $\omega_0 = \frac{1}{\sqrt{LC}}$ , the impedance is purely real (phase angle 0°)

$$\underline{V_s} = \underline{I_s} \underline{Z}$$

$$|V_s| \angle \phi_v = |I_s| \angle \phi_i |Z| \angle \phi_z$$

to find a condition that lets  $V$  and  $I$  be in phase  
 $\rightarrow \phi_z$  must be zero  $\rightarrow$  meaning  $Z$  is purely real.
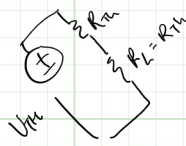
$$P_{max} = \frac{V_{th}^2}{4R_{th}} \Leftrightarrow$$


$\overset{S^1}{R_{th}} \Leftrightarrow R_{th}$   
 Deactivate sources only  
 for all independent circuit.